

ELECTRICAL ENGINEERING
FE Review Course
Outline

1. Electrostatics
 - a. Charge
 - b. Voltage
 - c. Current
 - d. Resistance
2. Circuit Analysis Basics
 - a. Resistor simplification
 - i. Parallel
 - ii. Series
 - b. Source Equivalents
 - i. Thevenin
 - ii. Norton
 - c. Node Analysis
 - d. Loop Analysis
3. Transient Circuits
 - a. RC Circuits
 - b. RL Circuits
4. AC Circuits
 - i. RMS
 - ii. Phasor Transforms
 - iii. AC impedance
 - iv. AC Steady State analysis
5. Power
 - a. DC Power
 - i. Power supplied
 - ii. Power Absorbed
 - b. AC Power
 - i. Complex power
 - ii. power factor
6. Transformers
 - a. Current and Voltage in an Ideal transformers
 - b. Impedance seen at the input of an ideal transformer
7. Operational Amplifiers (OP-AMPS)
 - a. Ideal OP-AMPS
 - b. solving OP-AMP Circuits
8. Resonant Circuits
 - a. Series Resonance
 - b. Parallel Resonance
 - c. Quality Factor
 - d. Bandwidth

What you need to know:

1. Electrostatics

a. Charge

- i. Units: Coulombs (C), 1 C is defined as the charge of 6.24×10^{16} electrons. The charge of an electron is 1.6×10^{-19} C.
- ii. The force of one charge on another charge: $\vec{F}_{12} = \frac{Q_1 Q_2}{4\pi\epsilon r^2} \vec{a}_{12}$;

Where:


1. Q_i = the i the point charge
 2. \vec{F}_{12} = the force on charge 2 due to charge 1
 3. r = the distance between the two charges
 4. \vec{a}_{12} = a unit vector directed from 1 to 2
 5. ϵ = the permittivity of the medium (how capable is the medium in which the charges exist of allowing these forces to exist)
- b. Voltage – The potential difference between two points, is the work done per unit charge required to move the charge between two points.

- c. Current – Rate of charge passing across a surface:

$$I = i(t) = \frac{dQ}{dt}$$

- d. Resistance – Measure of the ability of charge to move from one point to another for a given potential difference (voltage).

$$R = \frac{\rho L}{A}$$

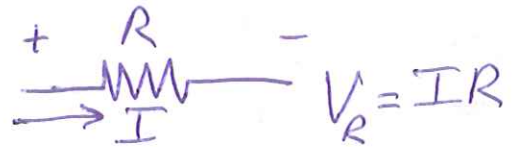

- e. Ohm's Law $V=IR$ or $v(t) = i(t)R$


2. Circuit Analysis

a. Resistor Simplification

- i. Two resistors in series: $R_{TOT} = R_1 + R_2$



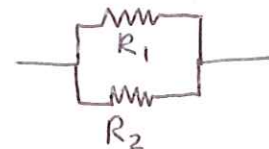- ii. Two resistors in parallel: $R_{TOT} = \frac{R_1 R_2}{R_1 + R_2}$



- b. Node Analysis – Using Kirchhoff's Current Law (KCL): ($\sum I = 0$) at any node.

$$\text{And: } I_{AB} = \frac{V_A - V_B}{R_{AB}}$$

Write a system of equations to solve for unknown node voltages.


- c. Loop Analysis – Using Kirchhoff's Voltage Law (KVL): ($\sum V = 0$) around any closed path.

Write a system of equations to solve for the unknown currents in each branch.

- d. Source equivalents – At any port a linear circuit can be simplified into an ideal source and a resistance

- i. Thevenin Equivalent Circuit – circuit is simplified into a series combination of an ideal voltage source and a resistance.

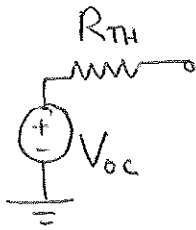
1. Find the open circuit voltage (V_{oc}) at the port of interest



2. Find the equivalent resistance (R_{TH}) at the port of interest
Or Find the short circuit current (I_{sc}) at the port of interest

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

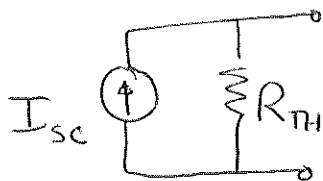- ii. Norton Equivalent Circuit – circuit is simplified into a parallel combination of an ideal current source and a resistance



1. Find the short circuit current (I_{sc}) at the port of interest
2. Find the equivalent resistance (R_{TH}) at the port of interest
Or Find the open circuit voltage (V_{oc}) at the port if interest

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

3. Transient Circuits – Circuits that contain capacitors and/or inductors as well as resistors. Voltages or Current sources are switched on or off at $t = 0$. Response is analyzed

- a. Capacitors: $C = \frac{\epsilon A}{d}$; capacitance for a parallel plate capacitor



$$i(t) = C \frac{dv_c(t)}{dt}$$


open ckt to DC

- b. Inductors: $L = \frac{N\phi}{i(t)}$;

inductance for a coil with N turns and magnetic flux ϕ enclosed in the coil

L SHORT TO DC

$$v(t) = L \frac{di_L(t)}{dt}$$

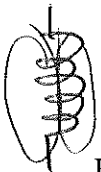

Requires solving first order (C or L only) or second order (L and C) differential eqns.

4. AC Circuits – Steady state analysis of circuits with (periodic) sinusoidal voltage and current sources.

$$\omega = 2\pi f$$

- a. Capacitors replaced with frequency dependent impedance $Z_C = \frac{1}{j\omega C}$
- b. Inductors replaced with frequency dependent impedance $Z_L = j\omega L$
- c. Circuit Analysis is simplified from DIFFEQ's to (complex) algebraic techniques used in resistive circuit analysis

5. Power

- a. DC (Resistive) Circuits

- i. Real power P supplied by a source; $P = VI$
- ii. Power absorbed by a resistor; $P = \frac{V^2}{R} = I^2 R$
- iii. Circuits with multiple sources may have some sources ABSORBING power. (Battery charging)

- b. AC (Complex) Circuits

Complex power; $S = P + jQ$

$$\begin{aligned} \text{Real Power } P &= \left(\frac{1}{2}\right) V_{max} I_{max} \cos\theta \\ &= V_{rms} I_{rms} \cos\theta \end{aligned}$$


$$\text{Complex Power } Q = \left(\frac{1}{2}\right) V_{max} I_{max} \sin\theta$$

θ is the angle measured from V to I.

6. Transformers: Two coils in proximity sharing magnetic flux.

$$n = \frac{N_1}{N_2} ; \text{ the ratio of the number of turns in the two coils}$$

$$n = \frac{|V_1|}{|V_2|} = \frac{|I_2|}{|I_1|}$$

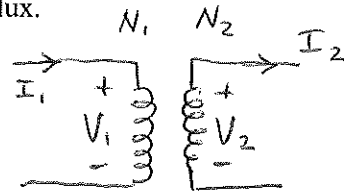


Beware of the Dots!

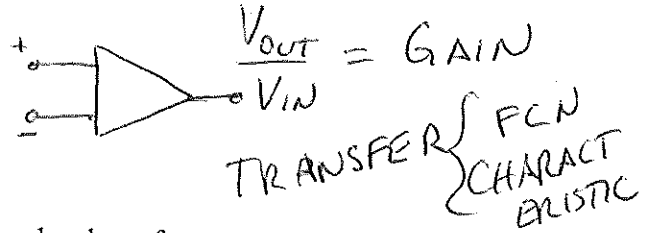- ## 7. Operational Amplifiers

For Ideal Op-Amps:

- No current flows into the input terminals
- The input terminals have the same voltage



8. Resonant Circuits – Parallel and Series LC circuits have a bandpass frequency response. This response is located at a center frequency (ω_o) and has a bandwidth (BW)

Resonant Frequency: $\omega_o = \frac{1}{\sqrt{LC}}$

Impedance at Resonance: $Z = R$

Series Resonance: $Z_L + Z_C = 0$

Parallel Resonance: $\infty = Z_L \parallel Z_C$


a fun of ω

$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC}$

$BW = \frac{\omega_o}{Q}$

$Q = \omega_o RC = \frac{R}{\omega_o L}$

Quality Factor


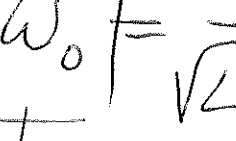


V_L as a fn of w

 $V_L @ DC$

$$V_L = I Z_L$$

$$V_L(\omega) \Big|_{\omega=0} = I_f \omega L = 0$$

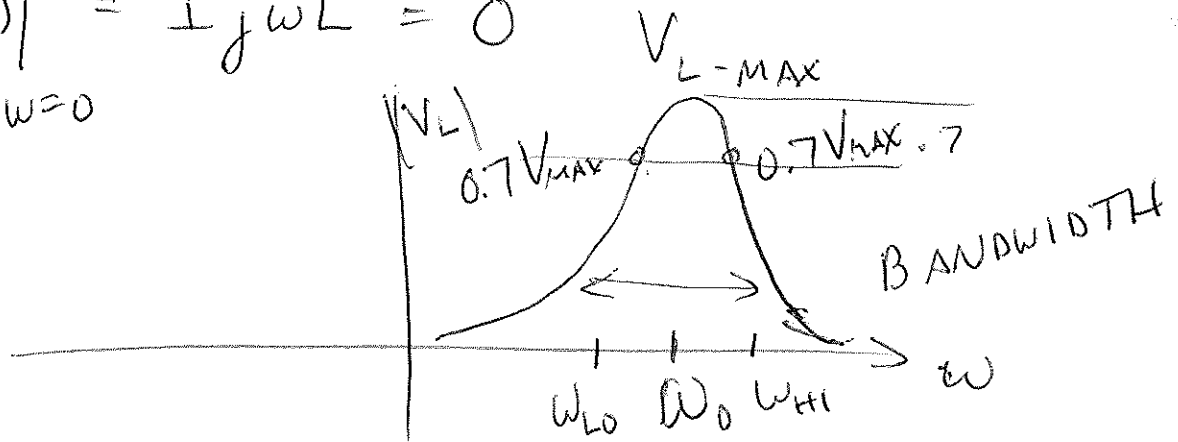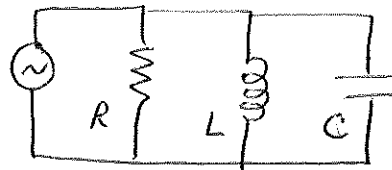

ELECTRIC CIRCUITS

UNITS

The basic electrical units are coulombs for charge, volts for voltage, amperes for current, and ohms for resistance and impedance.

ELECTROSTATICS

$$\mathbf{F}_2 = \frac{Q_1 Q_2}{4\pi\epsilon r^2} \mathbf{a}_{r12}, \text{ where}$$

\mathbf{F}_2 = the force on charge 2 due to charge 1,

Q_i = the i th point charge,

r = the distance between charges 1 and 2,

\mathbf{a}_{r12} = a unit vector directed from 1 to 2, and

ϵ = the permittivity of the medium.

For free space or air:

$$\epsilon = \epsilon_0 = 8.85 \times 10^{-12} \text{ Farads/meter}$$

Electrostatic Fields

Electric field intensity \mathbf{E} (volts/meter) at point 2 due to a point charge Q_1 at point 1 is

$$\mathbf{E} = \frac{Q_1}{4\pi\epsilon r^2} \mathbf{a}_{r12}$$

For a line charge of density ρ_L C/m on the z -axis, the radial electric field is

$$\mathbf{E}_L = \frac{\rho_L}{2\pi\epsilon r} \mathbf{a}_r$$

For a sheet charge of density ρ_s C/m² in the x - y plane:

$$\mathbf{E}_s = \frac{\rho_s}{2\epsilon} \mathbf{a}_z, z > 0$$

Gauss' law states that the integral of the electric flux density $\mathbf{D} = \epsilon\mathbf{E}$ over a closed surface is equal to the charge enclosed or

$$Q_{\text{enc}} = \oint_{sv} \epsilon \mathbf{E} \cdot d\mathbf{S}$$

The force on a point charge Q in an electric field with intensity \mathbf{E} is $\mathbf{F} = Q\mathbf{E}$.

The work done by an external agent in moving a charge Q in an electric field from point p_1 to point p_2 is

$$W = -Q \int_{p_1}^{p_2} \mathbf{E} \cdot d\mathbf{l}$$

The energy stored W_E in an electric field \mathbf{E} is

$$W_E = (1/2) \int_V \epsilon |\mathbf{E}|^2 dv$$

Voltage

The potential difference V between two points is the work per unit charge required to move the charge between the points.

For two parallel plates with potential difference V , separated by distance d , the strength of the \mathbf{E} field between the plates is

$$E = \frac{V}{d}$$

directed from the + plate to the - plate.

Current

Electric current $i(t)$ through a surface is defined as the rate of charge transport through that surface or

$$i(t) = dq(t)/dt, \text{ which is a function of time } t$$

since $q(t)$ denotes instantaneous charge.

A constant current $i(t)$ is written as I , and the vector current density in amperes/m² is defined as \mathbf{J} .

Magnetic Fields

For a current carrying wire on the z -axis

$$\mathbf{H} = \frac{\mathbf{B}}{\mu} = \frac{I \mathbf{a}_\phi}{2\pi r}, \text{ where}$$

\mathbf{H} = the magnetic field strength (amperes/meter),

\mathbf{B} = the magnetic flux density (tesla),

\mathbf{a}_ϕ = the unit vector in positive ϕ direction in cylindrical coordinates,

I = the current, and

μ = the permeability of the medium.

For air: $\mu = \mu_0 = 4\pi \times 10^{-7}$ H/m

Force on a current carrying conductor in a uniform magnetic field is

$$\mathbf{F} = I\mathbf{L} \times \mathbf{B}, \text{ where}$$

\mathbf{L} = the length vector of a conductor.

The energy stored W_H in a magnetic field \mathbf{H} is

$$W_H = (1/2) \int_V \mu |\mathbf{H}|^2 dv$$

Induced Voltage

Faraday's Law; For a coil of N turns enclosing flux ϕ :

$$v = -N d\phi/dt, \text{ where}$$

v = the induced voltage, and

ϕ = the flux (webers) enclosed by the N conductor turns, and

$$\phi = \int_S \mathbf{B} \cdot d\mathbf{S}$$

Resistivity

For a conductor of length L , electrical resistivity ρ , and area A , the resistance is

$$R = \frac{\rho L}{A}$$

For metallic conductors, the resistivity and resistance vary linearly with changes in temperature according to the following relationships:

$$\rho = \rho_0 [1 + \alpha (T - T_0)], \text{ and}$$

$$R = R_0 [1 + \alpha (T - T_0)], \text{ where}$$

ρ_0 is resistivity at T_0 , R_0 is the resistance at T_0 , and

α is the temperature coefficient.

Ohm's Law: $V = IR$; $v(t) = i(t) R$

Resistors in Series and Parallel

For series connections, the current in all resistors is the same and the equivalent resistance for n resistors in series is

$$R_T = R_1 + R_2 + \dots + R_n$$

For parallel connections of resistors, the voltage drop across each resistor is the same and the resistance for n resistors in parallel is

$$R_T = 1/(1/R_1 + 1/R_2 + \dots + 1/R_n)$$

For two resistors R_1 and R_2 in parallel

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

Power in a Resistive Element

$$P = VI = \frac{V^2}{R} = I^2 R$$

Kirchhoff's Laws

Kirchhoff's voltage law for a closed path is expressed by


$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$

Kirchhoff's current law for a closed surface is


$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

SOURCE EQUIVALENTS

For an arbitrary circuit

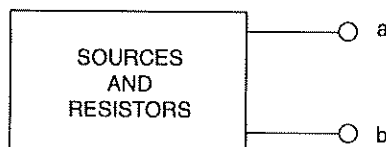


The Thévenin equivalent is

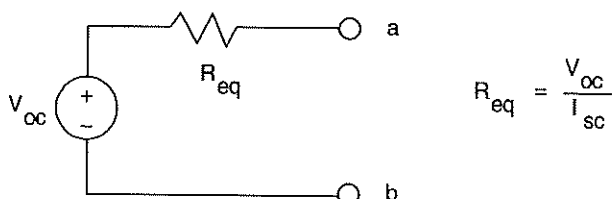


The open circuit voltage V_{oc} is $V_a - V_b$, and the short circuit current is I_{sc} from a to b .

The Norton equivalent circuit is

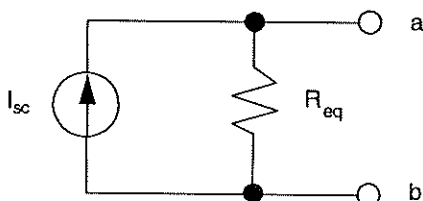

where I_{sc} and R_{eq} are defined above.

A load resistor R_L connected across terminals a and b will draw maximum power when $R_L = R_{eq}$.

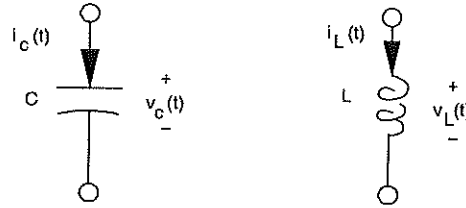CAPACITORS AND INDUCTORS

The charge $q_C(t)$ and voltage $v_C(t)$ relationship for a capacitor C in farads is

$$C = q_C(t)/v_C(t) \quad \text{or} \quad q_C(t) = C v_C(t)$$

A parallel plate capacitor of area A with plates separated a distance d by an insulator with a permittivity ϵ has a capacitance

$$C = \frac{\epsilon A}{d}$$

The current-voltage relationships for a capacitor are

$$v_C(t) = v_C(0) + \frac{1}{C} \int_0^t i_C(\tau) d\tau$$

and $i_C(t) = C (dv_C/dt)$

The energy stored in a capacitor is expressed in joules and given by

$$\text{Energy} = C v_C^2 / 2 = q_C^2 / 2C = q_C v_C / 2$$

The inductance L of a coil is

$$L = N\phi/i_L$$

and using Faraday's law, the voltage-current relations for an inductor are

$$v_L(t) = L (di_L/dt)$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(\tau) d\tau, \text{ where}$$

v_L = inductor voltage,

L = inductance (henrys), and

i = current (amperes).

The energy stored in an inductor is expressed in joules and given by

$$\text{Energy} = L i_L^2 / 2$$

Capacitors and Inductors in Parallel and Series

Capacitors in Parallel

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

Capacitors in Series

$$C_{eq} = \frac{1}{1/C_1 + 1/C_2 + \dots + 1/C_n}$$


Inductors in Parallel

$$L_{eq} = \frac{1}{1/L_1 + 1/L_2 + \dots + 1/L_n}$$

Inductors in Series

$$L_{eq} = L_1 + L_2 + \dots + L_n$$


RC AND RL TRANSIENTS

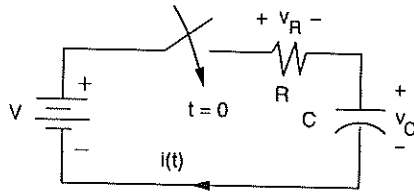

$$t \geq 0; v_C(t) = v_C(0)e^{-t/RC} + V(1 - e^{-t/RC})$$

$$i(t) = \{[V - v_C(0)]/R\}e^{-t/RC}$$
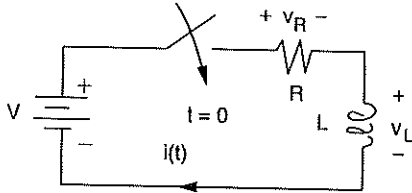
$$v_R(t) = i(t)R = [V - v_C(0)]e^{-t/RC}$$



$$t \geq 0; i(t) = i(0)e^{-Rt/L} + \frac{V}{R}(1 - e^{-Rt/L})$$

$$v_R(t) = i(t)R = i(0)R e^{-Rt/L} + V(1 - e^{-Rt/L})$$

$$v_L(t) = L(di/dt) = -i(0)R e^{-Rt/L} + V e^{-Rt/L}$$

where $v(0)$ and $i(0)$ denote the initial conditions and the parameters RC and L/R are termed the respective circuit time constants.

OPERATIONAL AMPLIFIERS

$$v_o = A(v_1 - v_2)$$


where

A is large ($> 10^4$), and

$v_1 - v_2$ is small enough so as not to saturate the amplifier.

For the ideal operational amplifier, assume that the input currents are zero and that the gain A is infinite so when operating linearly $v_2 - v_1 = 0$.

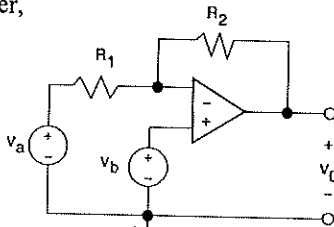For the two-source configuration with an ideal operational amplifier,



$$v_o = -\frac{R_2}{R_1}v_a + \left(1 + \frac{R_2}{R_1}\right)v_b$$

If $v_a = 0$, we have a non-inverting amplifier with

$$v_o = \left(1 + \frac{R_2}{R_1}\right)v_b$$

If $v_b = 0$, we have an inverting amplifier with

$$v_o = -\frac{R_2}{R_1}v_a$$

AC CIRCUITS

For a sinusoidal voltage or current of frequency f (Hz) and period T (seconds),

$$f = 1/T = \omega/(2\pi), \text{ where}$$

ω = the angular frequency in radians/s.

Average Value

For a periodic waveform (either voltage or current) with period T ,

$$X_{\text{ave}} = (1/T) \int_0^T x(t) dt$$

The average value of a full-wave rectified sine wave is

$$X_{\text{ave}} = (2X_{\text{max}})/\pi$$

and half this for a half-wave rectification, where

X_{max} = the peak amplitude of the waveform.

Effective or RMS Values

For a periodic waveform with period T , the rms or effective value is

$$X_{\text{rms}} = \left[(1/T) \int_0^T x^2(t) dt \right]^{1/2}$$

For a sinusoidal waveform and full-wave rectified sine wave,

$$X_{\text{rms}} = X_{\text{max}}/\sqrt{2}$$

For a half-wave rectified sine wave,

$$X_{\text{rms}} = X_{\text{max}}/2$$

Sine-Cosine Relations

$$\cos(\omega t) = \sin(\omega t + \pi/2) = -\sin(\omega t - \pi/2)$$

$$\sin(\omega t) = \cos(\omega t - \pi/2) = -\cos(\omega t + \pi/2)$$

Phasor Transforms of Sinusoids

$$P[V_{\text{max}} \cos(\omega t + \phi)] = V_{\text{rms}} \angle \phi = V$$

$$P[I_{\text{max}} \cos(\omega t + \theta)] = I_{\text{rms}} \angle \theta = I$$

For a circuit element, the impedance is defined as the ratio of phasor voltage to phasor current.

$$Z = \frac{V}{I}$$

For a Resistor,

$$Z_R = R$$

For a Capacitor,

$$Z_C = \frac{1}{j\omega C} = jX_C$$

For an Inductor,

$$Z_L = j\omega L = jX_L, \text{ where}$$

X_C and X_L are the capacitive and inductive reactances respectively defined as

$$X_C = -\frac{1}{\omega C} \quad \text{and} \quad X_L = \omega L$$

Impedances in series combine additively while those in parallel combine according to the reciprocal rule just as in the case of resistors.

Complex Power

Real power P (watts) is defined by

$$P = (1/2)V_{\max}I_{\max} \cos \theta$$

$$= V_{\text{rms}}I_{\text{rms}} \cos \theta$$

where θ is the angle measured from V to I . If I leads (lags) V , then the power factor ($p.f.$),

$$p.f. = \cos \theta$$

is said to be a leading (lagging) $p.f.$

Reactive power Q (vars) is defined by

$$Q = (1/2)V_{\max}I_{\max} \sin \theta$$

$$= V_{\text{rms}}I_{\text{rms}} \sin \theta$$

Complex power S (volt-amperes) is defined by

$$S = VI^* = P + jQ,$$

where I^* is the complex conjugate of the phasor current.

For resistors, $\theta = 0$, so the real power is

$$P = V_{\text{rms}}I_{\text{rms}} = V_{\text{rms}}^2/R = I_{\text{rms}}^2R$$

RESONANCE

The radian resonant frequency for both parallel and series resonance situations is

$$\omega_o = \frac{1}{\sqrt{LC}} = 2\pi f_o \text{ (rad/s)}$$

Series Resonance

$$\omega_o L = \frac{1}{\omega_o C}$$

$$Z = R \text{ at resonance.}$$

$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o CR}$$

$$BW = \omega_o/Q \text{ (rad/s)}$$


Parallel Resonance

$$\omega_o L = \frac{1}{\omega_o C} \text{ and}$$

$$Z = R \text{ at resonance.}$$

$$Q = \omega_o RC = \frac{R}{\omega_o L}$$

$$BW = \omega_o/Q \text{ (rad/s)}$$

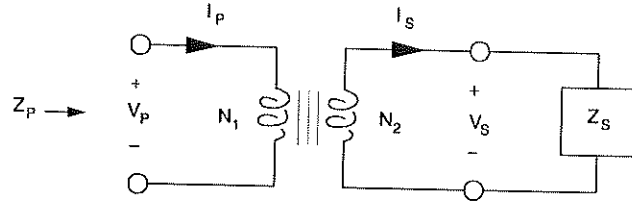TRANSFORMERS**Turns Ratio**

$$a = N_1/N_2$$

$$a = \left| \frac{V_p}{V_s} \right| = \left| \frac{I_s}{I_p} \right|$$

The impedance seen at the input is

$$Z_p = a^2 Z_s$$

ALGEBRA OF COMPLEX NUMBERS

Complex numbers may be designated in rectangular form or polar form. In rectangular form, a complex number is written in terms of its real and imaginary components.

$$z = a + jb, \text{ where}$$

a = the real component,

b = the imaginary component, and

$$j = \sqrt{-1}$$

In polar form

$$z = c \angle \theta, \text{ where}$$

$$c = \sqrt{a^2 + b^2},$$

$$\theta = \tan^{-1}(b/a),$$

$$a = c \cos \theta, \text{ and}$$

$$b = c \sin \theta.$$

Complex numbers are added and subtracted in rectangular form. If

$$z_1 = a_1 + jb_1 = c_1 (\cos \theta_1 + j \sin \theta_1)$$

$$= c_1 \angle \theta_1 \text{ and}$$

$$z_2 = a_2 + jb_2 = c_2 (\cos \theta_2 + j \sin \theta_2)$$

$$= c_2 \angle \theta_2, \text{ then}$$

$$z_1 + z_2 = (a_1 + a_2) + j(b_1 + b_2) \text{ and}$$

$$z_1 - z_2 = (a_1 - a_2) + j(b_1 - b_2)$$

While complex numbers can be multiplied or divided in rectangular form, it is more convenient to perform these operations in polar form.

$$z_1 \times z_2 = (c_1 \times c_2) \angle \theta_1 + \theta_2$$

$$z_1/z_2 = (c_1/c_2) \angle \theta_1 - \theta_2$$

The complex conjugate of a complex number $z_1 = (a_1 + jb_1)$ is defined as $z_1^* = (a_1 - jb_1)$. The product of a complex number and its complex conjugate is $z_1 z_1^* = a_1^2 + b_1^2$.

ELECTROSTATICS


CHARGE : UNIT IS COULOMB

- 1 electron has a charge of $1.6 \times 10^{-19} \text{ C}$
- 1 Coulomb is the charge of $6.24 \times 10^{16} \text{ e}$

FORCE

A FORCE OF ONE CHARGE ON ANOTHER
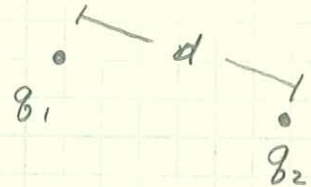
$$\vec{F}_{12} = \frac{q_1 q_2}{4\pi\epsilon d^2} \vec{a}_{12}$$



$q_i \equiv i^{\text{th}}$ POINT CHARGE COULOMBS

$\epsilon :=$ PERMITTIVITY OF THE MEDIUM (HOW CAPABLE IS THE MATERIAL WHERE THE CHARGE EXISTS TO ALLOW THE FORCES TO EXIST)

FREE SPACE VS TEFLON, METALS

$d :=$ distance between two charges q_1, q_2

$\vec{a}_{12} :=$ UNIT VECTOR FROM q_1 TO q_2


ELECTRIC FIELD

$$\vec{F}_{12} = q_1 \vec{E}$$

$$\vec{E}_2 = \frac{q_2}{4\pi\epsilon r^2} \vec{r}$$

ELECTRIC FIELD SURROUNDING A CHARGE

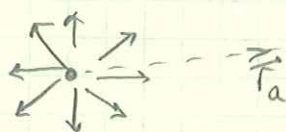$\vec{r} :=$ UNIT VECTOR POINTING FROM THE CHARGE TO THE
 \vec{E} FIELD EVALUATION POINT




CHARGE

EVALUATION POINT "a"

$$\vec{E}_a = \frac{q}{4\pi\epsilon d^2} \vec{r}_a$$


ANALOGY OF FLUID FLOW AND CURRENT FLOW

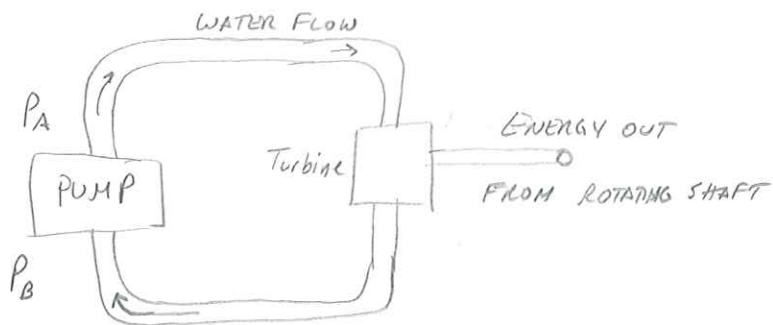

WATER EXITS PUMP AT HIGHER PRESSURE P_A
 WATER ENTERS PUMP AT LOWER PRESSURE P_B

FLOW RATE INTO TURBINE =
 FLOW RATE OUT




PRESSURE INTO TURBINE > PRESSURE OUT

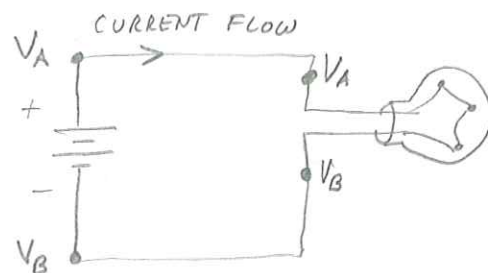

CURRENT EXITS BATTERY FROM
 HIGHER VOLTAGE
 CURRENT ENTERS BATTERY AT
 LOWER VOLTAGE

CURRENT INTO BULB = CURRENT OUT
 VOLTAGE IN \geq VOLTAGE OUT

FLOW RATE ANALOGY TO CURRENT FLOW :

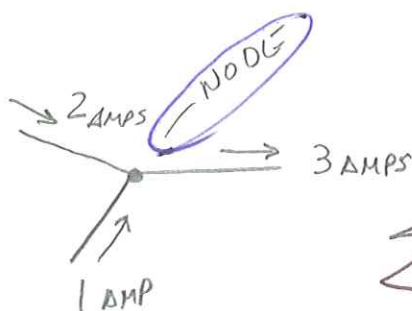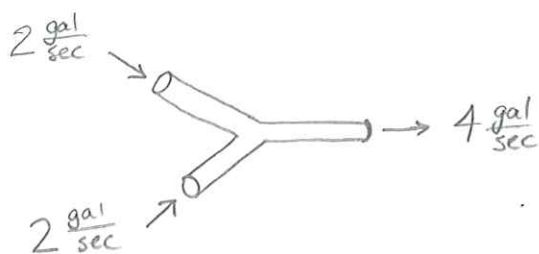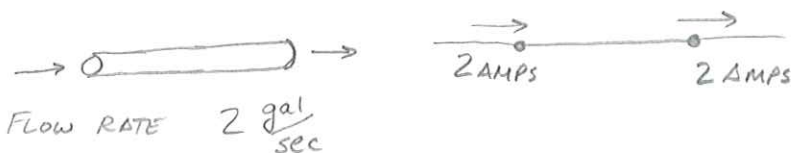


KCL

$$\sum i = 0$$

$$I_{IN} = I_{OUT}$$

KVL FOR A CLOSED PATH

$$\sum V_{rises} = \sum V_{drops}$$

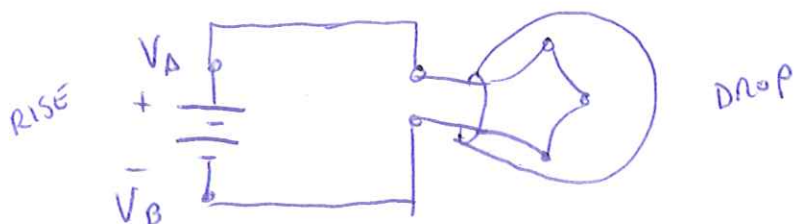

VOLTAGE POTENTIAL DIFFERENCE BTWN 2 POINTS

WORK DONE PER UNIT CHARGE REQ'D TO MOVE CHARGE BTWN 2 POINTS

POINT A

POINT B



$$V_A - V_B = \int_a^b \vec{E} \cdot d\vec{l}$$

LINE INTEGRAL OF \vec{E}

CURRENT

RATE OF CHANGE PASSING ACROSS A SURFACE OF POSITIVE CHARGE.

$$I = i(t) = \frac{dQ}{dt}$$


RESISTANCE

MEASURES ABILITY OF CHARGE TO MOVE FROM ONE POINT TO ANOTHER

$$R = \frac{\rho L}{A}$$

ρ := MATERIAL RESISTIVITY

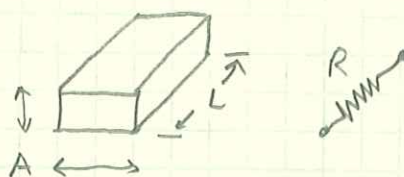
$$\sigma = \frac{1}{\rho} \text{ := CONDUCTIVITY}$$



OHMS LAW

DC
 $V = IR$

AC
 $v(t) = i(t) R$

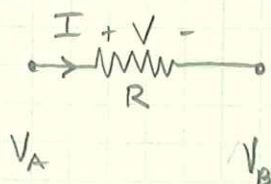

$$V_R = V_A - V_B$$

"VOLTAGE DROP ACROSS R."

PASSIVE SIGN CONVENTION: POSITIVE CHARGE FLOWS FROM HIGH VOLTAGE TO LOW.


SOLVING ELECTRIC CIRCUITS

SIMILAR TO A MECHANICAL SYSTEM WE SET UP A COORDINATE SYSTEM THAT WILL ESTABLISH THE POSITIVE DIRECTION.


AFTER CALCULATING VELOCITY (FOR EXAMPLE) IF THE ANSWER IS A POSITIVE NUMBER, OUR ARBITRARY SELECTION OF THE POSITIVE DIRECTION WERE CORRECT.

IF THE ANSWER WAS NEGATIVE, THIS MEANS MOVEMENT IS ACTUALLY IN THE OPPOSITE DIRECTION.

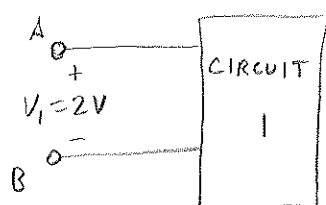
FOR ELECTRIC CKTS WE WILL ALSO ASSIGN AN ARBITRARY DIRECTION OF CURRENT FLOW AND VOLTAGE DIFFERENCE (POLARITY)



TERMINAL A IS 2V HIGHER THAN TERMINAL B

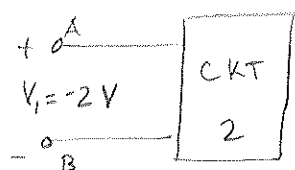


TERMINAL B IS 2V HIGHER THAN TERMINAL A

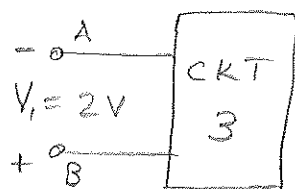

TERMINAL B IS 2V HIGHER THAN TERMINAL A

POWER DELIVERED VS. POWER ABSORBED

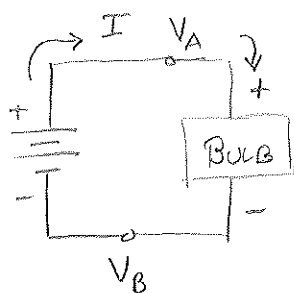

BATTERY DELIVERS POWER TO BULB

BULB ABSORBS POWER FROM BATTERY

CONVENTION FOR CURRENT

POSITIVE CURRENT IS THE FLOW OF POSITIVE CHARGE (OPPOSITE OF ELECTRON FLOW)

NEGATIVE CURRENT IS THE OPPOSITE FLOW OF POSITIVE CHARGE.



BOTH BRANCHES HAVE CURRENT FLOW NODE A TO B

CONVENTION FOR VOLTAGE

VOLTAGE BETWEEN 2 POINTS IS THE DIFFERENCE IN THE ENERGY LEVEL OF A UNIT CHARGE LOCATED AT EACH OF THE TWO POINTS.



VOLTAGE BETWEEN NODE A AND B IS $V_{AB} = -V_{BA}$

ENERGY AT NODE A IS GREATER THAN THAT AT NODE B.


IF $V_{AB} = 5$ VOLTAGE AT NODE A IS 5 VOLTS MORE THAN

IF $V_{AB} = -5$ 5 VOLTS LESS THAN.

VOLTAGE AT GROUND ALWAYS = 0.

CONVENTION FOR POWER


POWER IS ABSORBED OR SUPPLIED.

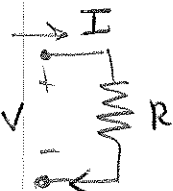


IF POSITIVE CURRENT FLOWS INTO A HIGHER VOLTAGE NODE : POWER IS ABSORBED

$$V = IR$$

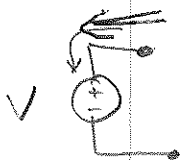IF POSITIVE CURRENT FLOWS OUT OF A HIGHER VOLTAGE NODE : POWER IS SUPPLIED.




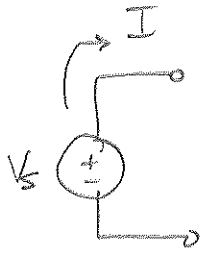FIND POWER ABSORBED/SUPPLIED BY EACH ELEMENT.




$$\text{POWER SUPPLIED} = -VI$$

$$\text{ABSORBED} = -VI$$

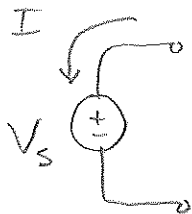


$$\text{POWER ABSORBED} = +VI$$

(CHARGING BATTERY)

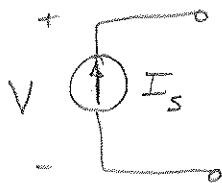


$$\text{POWER SUPPLIED} = +VI$$

$$\text{ABSORBED} = -VI$$

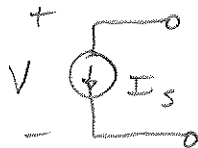

$$\text{POWER ABSORBED} = -VI$$

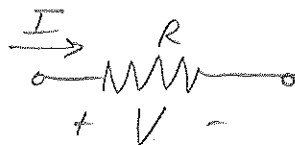

POWER ABSORBED.


$$P_A = VI$$

$$P_s = -VI$$

POWER ABSORBED


$$P = VI = v(t)i(t)$$

UNITS WATTS

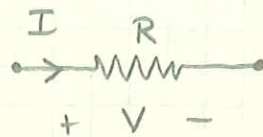

PASSIVE DEVICE ABSORBS "POSITIVE" POWER EQUAL TO CURRENT THROUGH TIMES VOLTAGE ACROSS.

<u>DC</u>	DIRECT	V	I	CONSTANT
<u>AC</u>	ALTERNATING	$v(t)$	$i(t)$	TIME VARYING

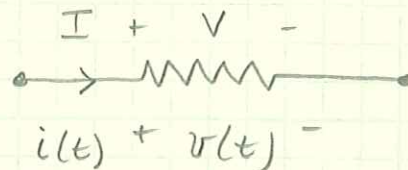

EX

$$V = 10 \text{ V} \quad I = 5 \text{ AMPS}$$

FIND R , POWER ABSORBED.

$$\text{SOLN} \quad V = IR$$

$$R = \frac{V}{I} = \underline{\underline{2 \Omega}}$$

$$P = VI = \underline{\underline{50 \text{ WATTS}}}$$

EX $v(t) = 10 \cos(t)$ $R = 2$

FIND $i(t)$ $P(t)$

$$\text{SOLN} \quad v(t) = i(t) R$$

$$i(t) = \frac{v(t)}{R} = 5 \cos(t) \text{ AMPS}$$

$$p(t) = 10 \cos(t) \times 5 \cos(t)$$

$$= 50 \cos^2(t) = 50 \left[\frac{1}{2} + \frac{1}{2} \cos(2t) \right]$$

$$p(t) = 25 + 25 \cos 2t \quad \text{WATTS}$$


↑
INSTANTANEOUS
POWER.

↑
AVERAGE POWER


$$P_{\text{AVE}} = \frac{VI}{2}$$

AC AVERAGE
POWER.

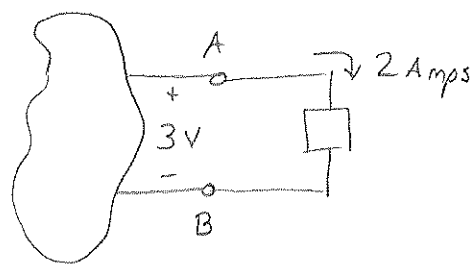- MORE COMPLICATED CRTS ARE NOT AS EASY TO PREDICT BEFORE PERFORMING CRT ANALYSIS.
- ONCE VOLTAGES AND CURRENTS ARE CALCULATED, WE CAN DETERMINE POWER DELIVERED AND ABSORBED.




POWER ABSORBED
(BVLB)

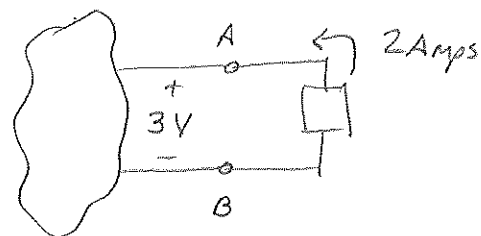


POWER SUPPLIED
(BATTERY)

CIRCUIT ELEMENTS

SOURCES : INDEPENDENT VOLTAGE SOURCE

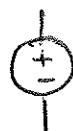


DC
CONSTANT

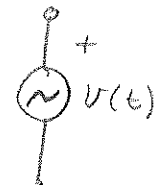


AC
SINUSOIDAL

INDEPENDENT CURRENT SOURCE

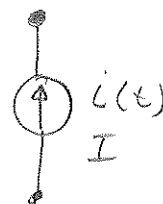


DEPENDENT SOURCES

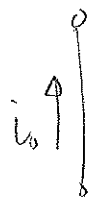

CURRENT

$$i = \beta i_0$$

$$i = g v_0$$

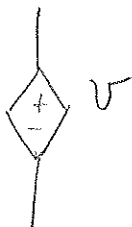


VOLTAGE

$$v = a v_0$$

$$v = r i_0$$
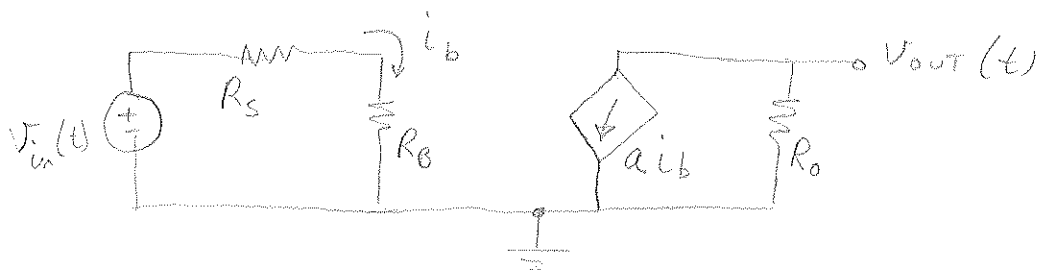
$$v_0 = \begin{matrix} + \\ \sqrt{v_0} \\ - \\ 0 \end{matrix}$$




SIMPLIFYING RESISTIVE CIRCUITS.

- RESISTOR SIMPLIFICATION
- THEVENIN EQUIVALENT CIRCUITS
- NORTON EQUIVALENT CIRCUITS.

RESISTORS IN SERIES




$$R_T = R_1 + R_2$$

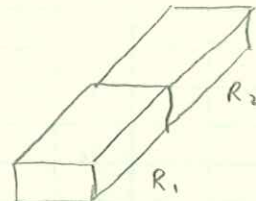


$$R = \frac{\rho L(2)}{A}$$

$$R = R_1 + R_2$$


RESISTORS IN PARALLEL

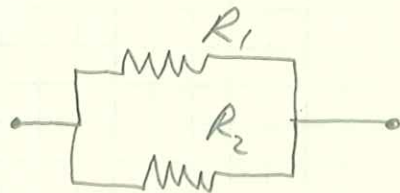


\Rightarrow

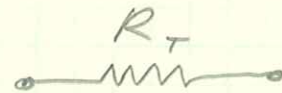

$$R_T = \frac{(R_1)(R_2)}{R_1 + R_2}$$

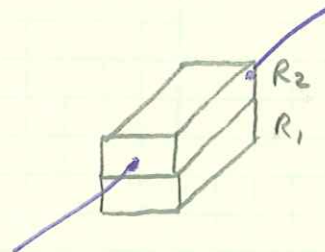

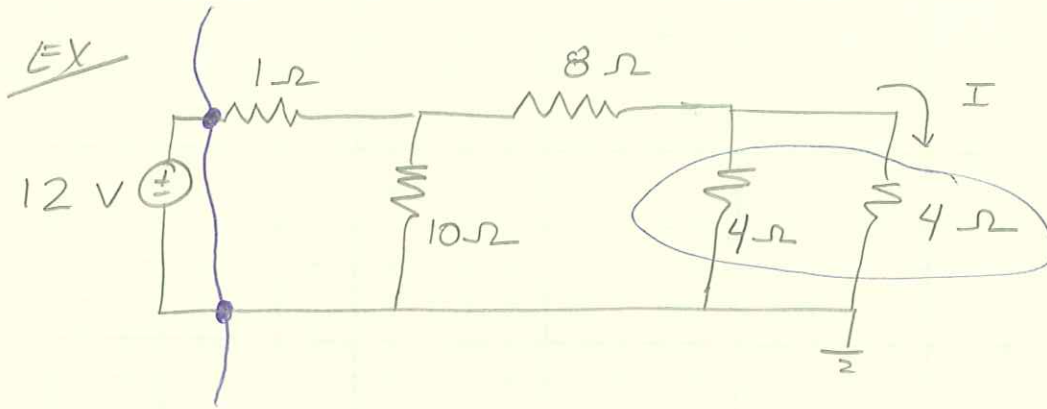
$$R_T = \frac{\rho L}{2A} = \frac{R_1}{2} = \frac{R_2}{2}$$






FIND I IN THIS CKT.

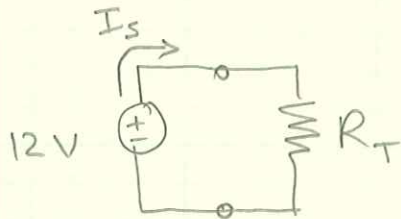CAN USE LOOP EQUATIONS OR RESISTIVE SIMPLIFICATION



CURRENT FROM SOURCE I_s
DELIVERED TO RESISTIVE CIRCUIT.
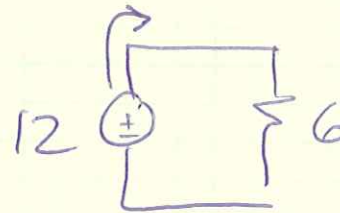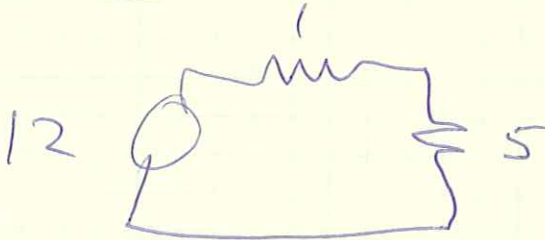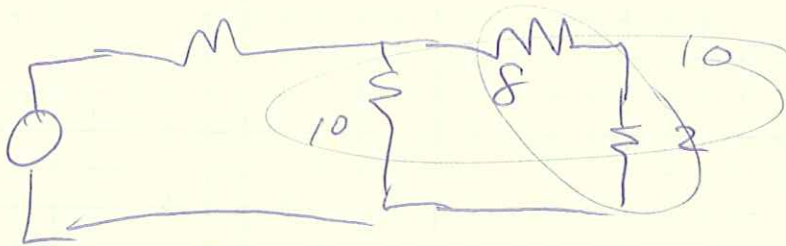
$$4\Omega // 4\Omega = \frac{16}{8} = 2\Omega$$





$$V = IR$$


$$\boxed{I = 2A}$$

THEVENIN AND NORTON EQUIVALENT CIRCUITS

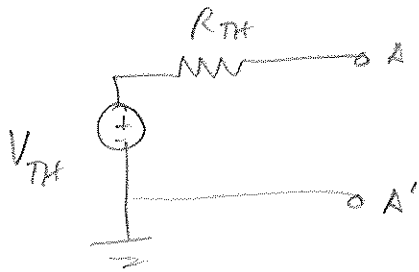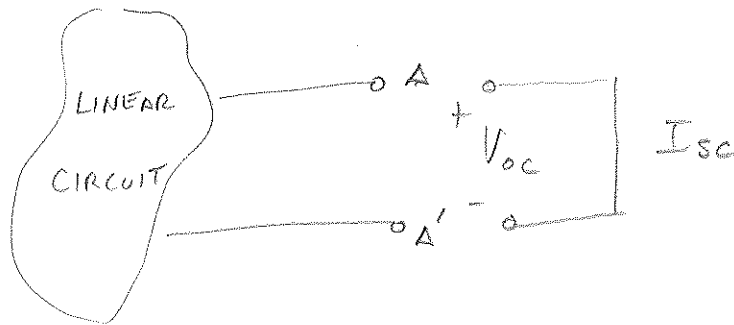AT ANY "PORT" OF A LINEAR CIRCUIT WE CAN REPLACE WITH AN IDEAL SOURCE AND A RESISTANCE



$$V_{OC} = V_{TH}$$

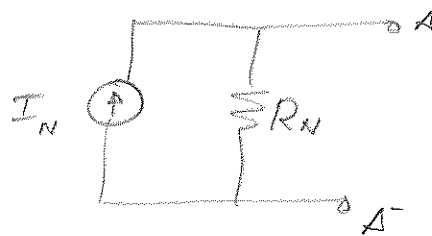

$$I_{SC} = I_N$$



$$R_{TH} = \frac{V_{SC}}{I_N}$$

Theremin


Porton

Equivalent Circuits

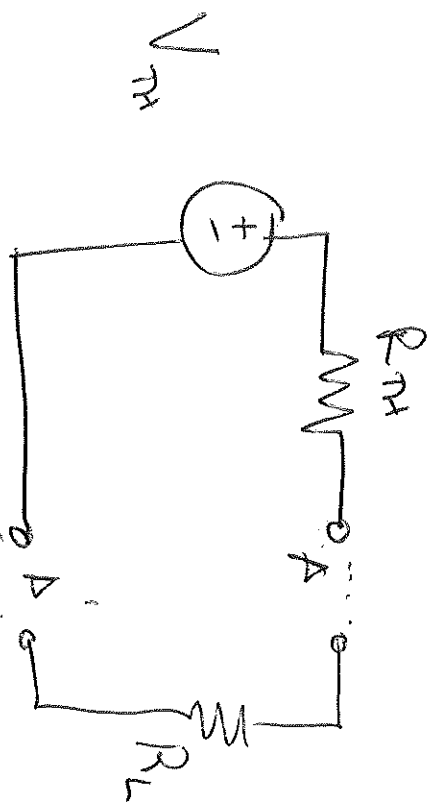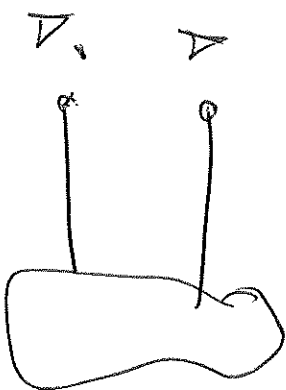AT ANY POINT OF A LINEAR CIRCUIT. WE CAN
REPLACE ALL ~~THE~~ ELEMENTS WITH IDEAL SOURCE
AND SINGLE RESISTANCE



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

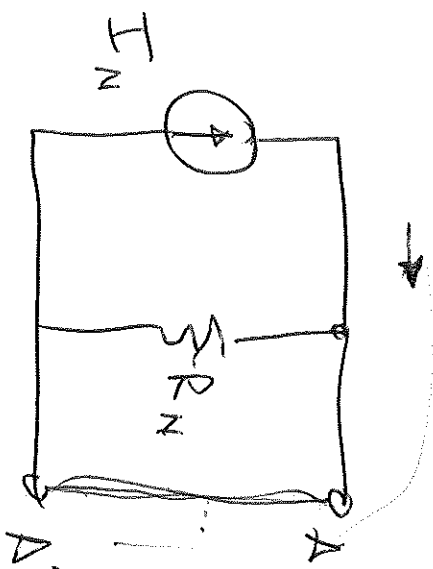

NEC.

AT NODE C


$$\sum I = 0$$

$$I_{Bc} + I_{Ac} + I_1 + I_{cN} = 0$$

ALL CURRENTS ARE POINTING INTO NODE C,

ONE OR MORE MUST BE NEGATIVE FOR KCL TO HOLD.

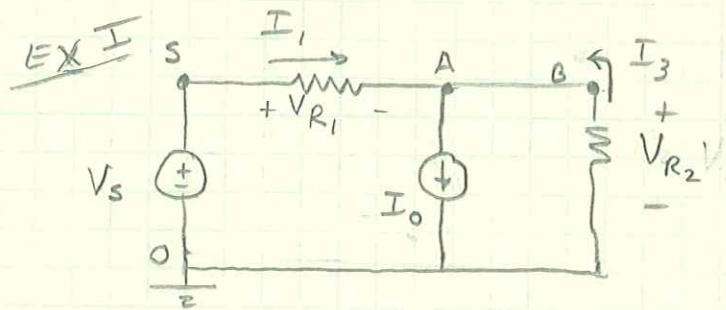* IF A CURRENT OR VOLTAGE ARE FOUND TO BE NEGATIVE, THEN ACTUAL $\{V, I\}$ IS OPPOSITE OF ORIGINAL ARBITRARY ASSIGNMENT.



FIND $I_1, I_2, V_B, V_A, V_{R_2}$

GIVEN
 $V_s = 5V \quad I_0 = 1A$

$$R_1 = 6\Omega \quad R_2 = 4\Omega$$

SOLN $I_1 + I_3 - I_0 = 0$
 $I_1 + I_3 = I_0 = 1A$

KCL @ A

$$I_1 = 1 - I_3$$

$$5 - V_{R_1} - V_{R_2} = 0$$

$$5 - I_1 R_1 + I_3 R_2 = 0$$

KVL

$$V_{R_2} = -I_3 R_2$$



NOTE PASSIVE SIGN CONVENTION

$$5 - (1 - I_3)R_1 + I_3 R_2 = 0$$

$$5 - 1R_1 + R_1 I_3 + R_2 I_3 = 0$$

$$10 I_3 = 1$$


$$I_3 = 0.1A$$

$$I_1 = 0.9A$$

$$V_B = -0.4V = -I_3 R_2$$

$$V_A = -0.4$$

EX II

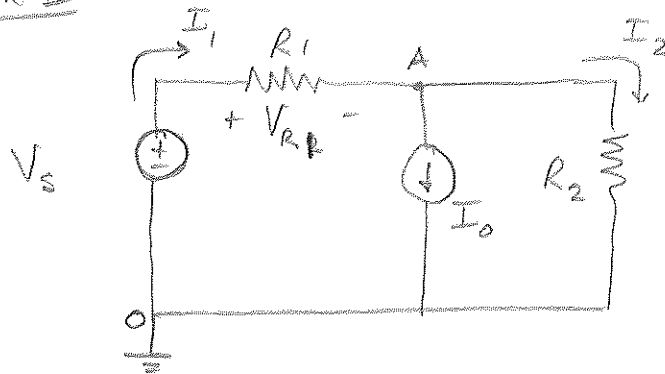

GIVEN

$$V_s = 5 \text{ V}$$

$$R_1 = 6 \Omega$$

$$I_0 = 1 \text{ A}$$

$$R_2 = 4 \Omega$$

FIND

$$I_1, I_2, V_B, V_{R2}$$

SOLUTION

KCL
@ A

$$I_1 - I_0 - I_2 = 0$$

$$I_1 = I_0 + I_2$$

$$I_1 = 1 + I_2$$

$$I_1 = 1 - \frac{1}{10}$$

$$I_1 = 0.9 \text{ A}$$

$$V_B = V_A = I_2 R_2 = \underline{\underline{-0.4 \text{ V}}}$$

$$V_{R2} = I_1 R_1 = \underline{\underline{5.4 \text{ V}}}$$

$$\text{KVL: } V_s - V_{R1} - V_{R2} = 0$$

$$V_s - I_1 R_1 - I_2 R_2 = 0$$

$$V_s - (1 + I_2) R_1 - I_2 R_2 = 0$$


$$V_s - R_1 - I_2 R_1 - I_2 R_2 = 0$$

$$I_2 = \frac{-(V_s - R_1)}{-(R_1 + R_2)}$$

$$I_2 = \frac{-(5 - 6)}{-(6 + 4)} = -\frac{1}{10} \text{ A}$$

$$I_2 = -\frac{1}{10} \text{ A}$$

FINDING POWER

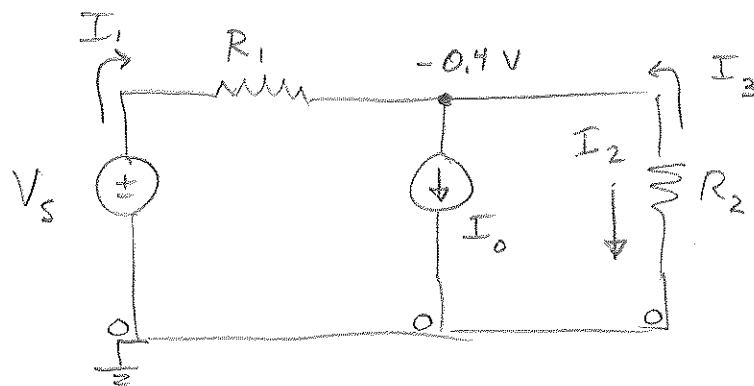

$$I_3 = -I_2 = 0.1 \text{ A}$$

$$V_A = -0.4 \text{ V}$$

$$V_S = 5 \text{ V}$$

$$I_1 = 0.9 \text{ A}$$

$$P_{V_S} = 5(0.9) = 4.5 \text{ W SUPPLIED}$$

$$P_{R_1} = VI = \frac{V^2}{R} = I^2 R_1 = (0.9)^2 6 = 4.86 \text{ W ABSORBED}$$

$$P_{R_2} = VI = (0.4)(0.1) = .04 \text{ W ABSORBED}$$


$$P_{I_0} = VI = (0.4)(1) = 0.4 \text{ W SUPPLIED}$$

$$\text{SUPPLIED} = \text{ABSORBED}$$

$$4.5 + .4 = 4.86 + .04$$

$$4.9 = 4.9$$

CONSERVED

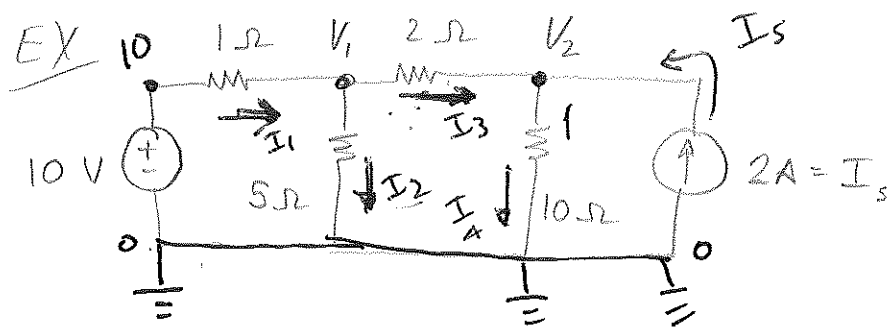

FIND ① V_1 V_2

② ALL BRANCH CURRENTS

③ POWER

SOLVE USING

KCL NODE ANALYSIS
VOLTAGE EQUATIONS

KVL LOOP ANALYSIS
CURRENT EQUATIONS

SUPERPOSITION

THEVENIN EQUIVALENT EQNS

KCL @ V_1

$$\frac{V_1 - 10}{1} + \frac{V_1}{5} + \frac{V_1 - V_2}{2} = 0$$

@ V_2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{10} - 2 = 0$$

SOLVE SIMULTANEOUSLY

$$10V_1 - 100 + 2V_1 + 5V_1 - 5V_2 = 0$$

$$17V_1 - 5V_2 = 100$$

$$V_1 = \frac{100 + 5V_2}{17}$$

$$5V_2 - 5V_1 + V_2 = 20$$

$$6V_2 - 5V_1 = 20$$

$$6V_2 - \frac{5}{17}(100 + 5V_2) = 20$$

$$102V_2 - 500 - 25V_2 = 340$$

$$77V_2 = 834$$


$$V_2 = \frac{834}{77} = 10.83$$

$$6(10.83) - 5V_1 = 20$$


$$V_1 = 9.0$$

SUPER POSITION (1 IND. SOURCE AT A TIME)


SET $I_s = 0$ (OPEN)

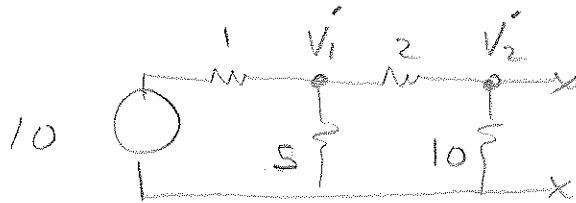


RESISTOR SIMPLIFICATION

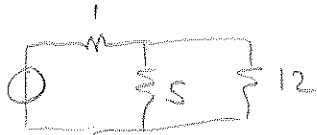

$$\frac{60}{17} = 3.53$$

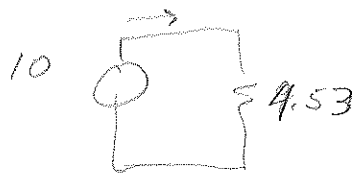

$$I = 2.21$$

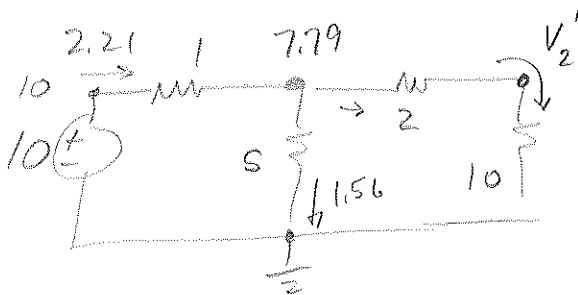



$$V_1' = 10 - 1(2.21) = 7.79$$

$$I_s' = \frac{7.79}{5} = 1.56$$

$$I_2' = 2.21 - 1.56$$


$$= 0.652$$

$$V_2' = 6.52V$$

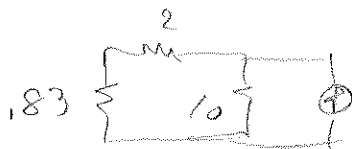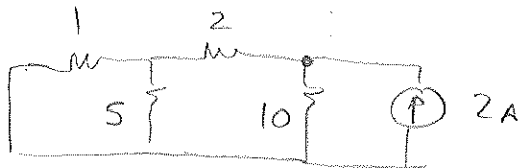


$$\frac{10(2.83)}{12.83}$$

$$2.2$$

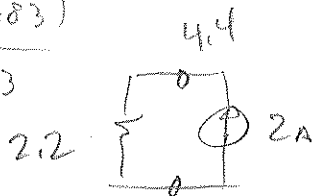

$$V_2'' = 4.4$$

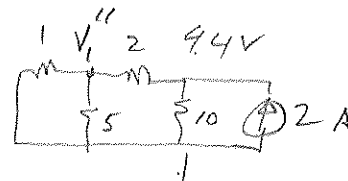

$$I_{10}'' = .44$$

$$-I_2'' = 2 - .44$$

$$= 1.56$$


$$V_1'' = 4.4V - (2)(1.56)$$

$$V_1'' = 0.88$$

$$V_2 = 6.52 + 4.4 = 10.9$$



$$V_1 = 7.79 + .88 = 8.7$$

THEVENIN EQUIVALENT

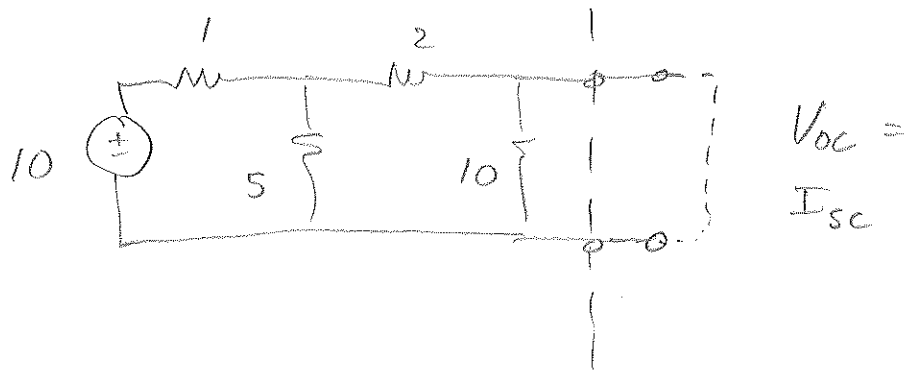


V_{OC} FOUND IN SUPERPOSITION = 6.52 V

FINDING I_{SC}

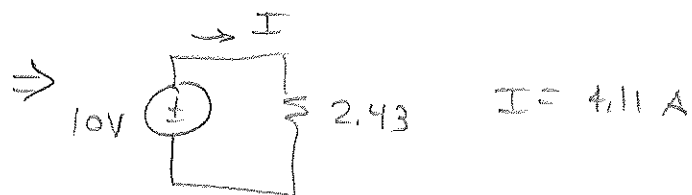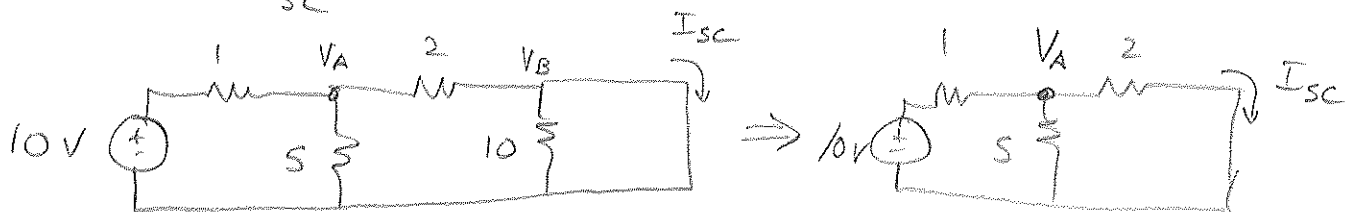


$$V_A = 10 - 1(4.11) = 5.89 \text{ V}$$
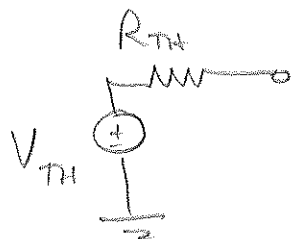
$$I_{SC} = \frac{5.89 \text{ V}}{2 \Omega} = \underline{\underline{2.95 \text{ A}}}$$



$$V_{TH} = V_{OC} = 6.52 \text{ V}$$
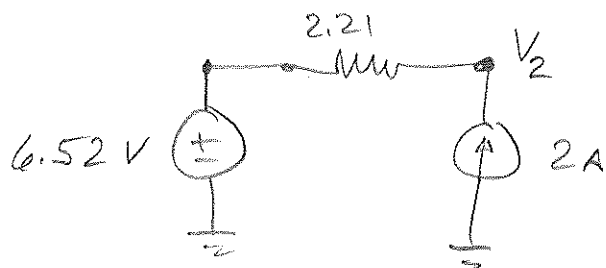
$$R_{TH} = \frac{V_{OC}}{I_{SC}} = 2.21 \Omega$$




$$V_2 = 6.52 + 2(2.21)$$

$$\boxed{V_2 = 10.9}$$


THEVENIN EQUIVALENT CIRCUIT

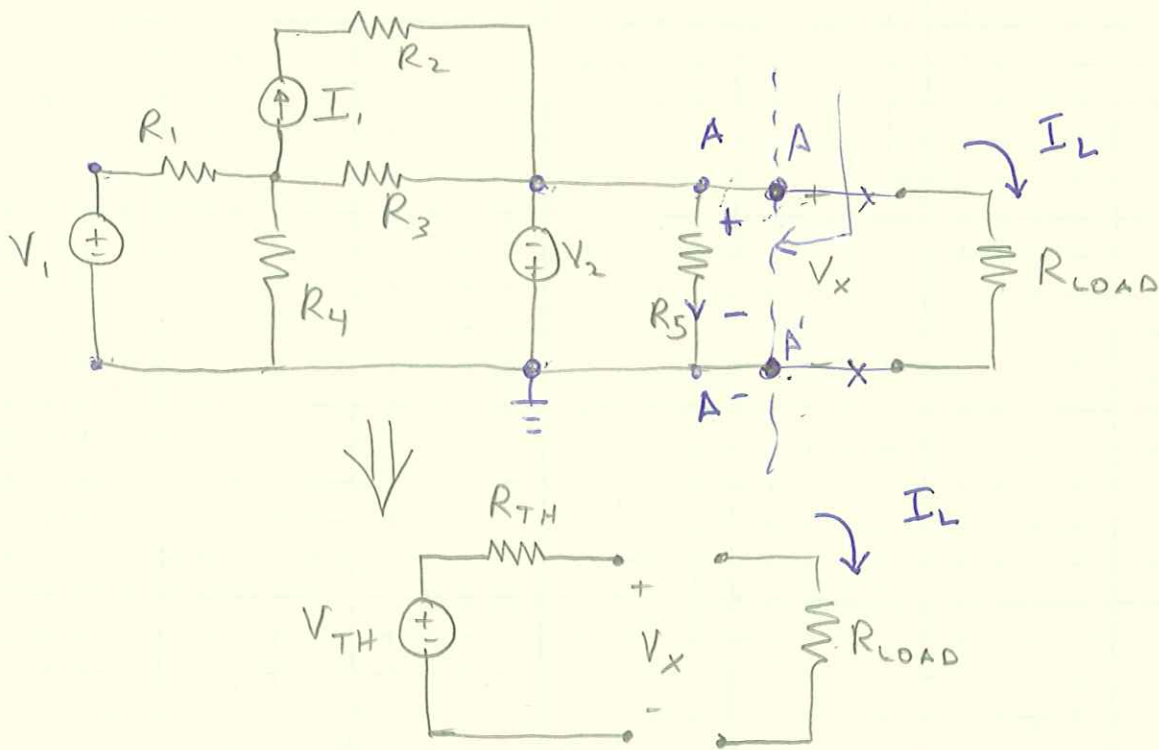ANY RESISTIVE CIRCUIT, NO MATTER HOW COMPLEX, CAN BE REDUCED TO A SERIES VOLTAGE AND RESISTANCE, AT ANY TERMINAL IN THAT CIRCUIT.




OR

NORTON EQUIVALENT.

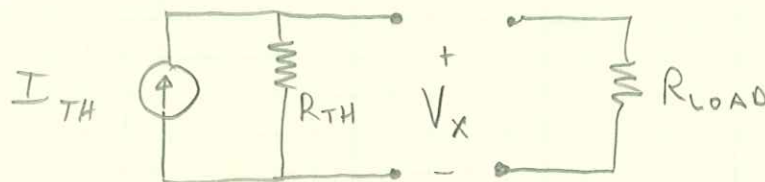
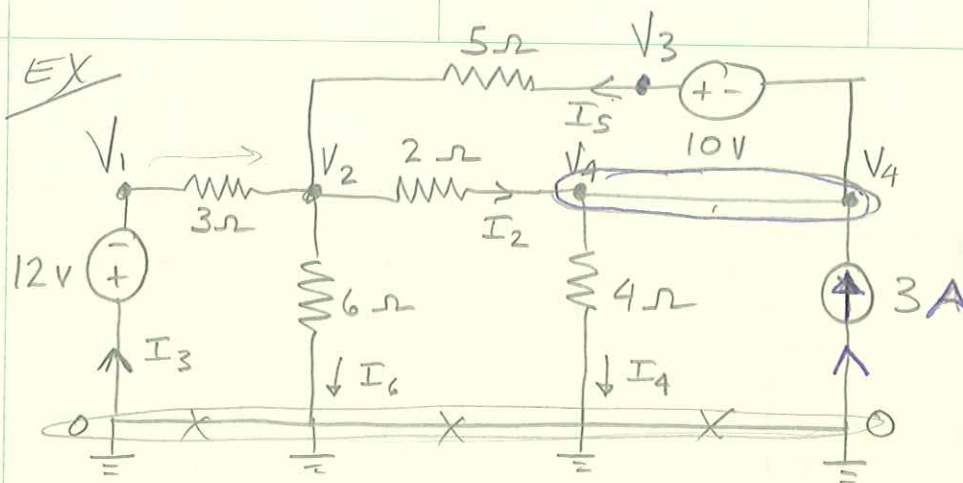
$$V_X = I_{TH} \left(\frac{R_{TH} R_L}{R_{TH} + R_L} \right)$$



FIND ALL BRANCH CURRENTS AND NODE VOLTAGES.

STEP 1) LABEL ALL BRANCHES AND NODES

BRANCH CURRENTS

I_3, I_6, I_4, I_5, I_2

FIND VOLTAGES AT ALL NODES
THEN USE OHM'S LAW

$$I_2 = \frac{V_2 - V_4}{2\Omega}$$

$$I_6 = \frac{V_2 - 0}{6}$$

$$V_1 = -12\text{ V}$$

$$V_3 = 10 + V_4$$

KCL @ NODE 2

$$I_3 + I_5 = I_6 + I_2$$

$$\sum I = 0$$

$$I_3 = \frac{V_1 - V_2}{3}$$

$$I_5 = \frac{V_3 - V_2}{5}$$

$$\frac{V_1 - V_2}{3} + \frac{V_3 - V_2}{5} = \frac{V_2}{6} + \frac{V_2 - V_4}{2}$$


KCL @ NODE 4

$$I_2 + 3 = I_4 + I_5$$

$$I_4 = \frac{V_4 - 0}{4}$$

4 EQN. 4 UNKNOWN CAN BE SOLVED SIMULTANEOUSLY

FIND V_{oc}

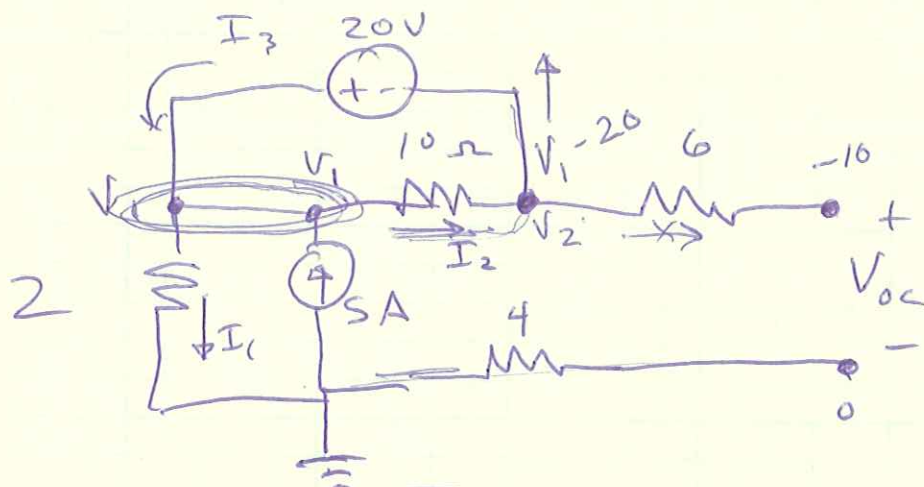

KCL @ V_1 $\boxed{I_2 + I_1 = 5 + I_3}$


$$\frac{V_1 - (V_1 - 20)}{10} + \frac{V_1 - 0}{2} = 5 + I_2$$

$$\boxed{\frac{V_1}{2} = 5}$$

$$V_1 = 10$$

$$\boxed{V_2 = -10}$$

$$\boxed{V_{oc} = -10}$$

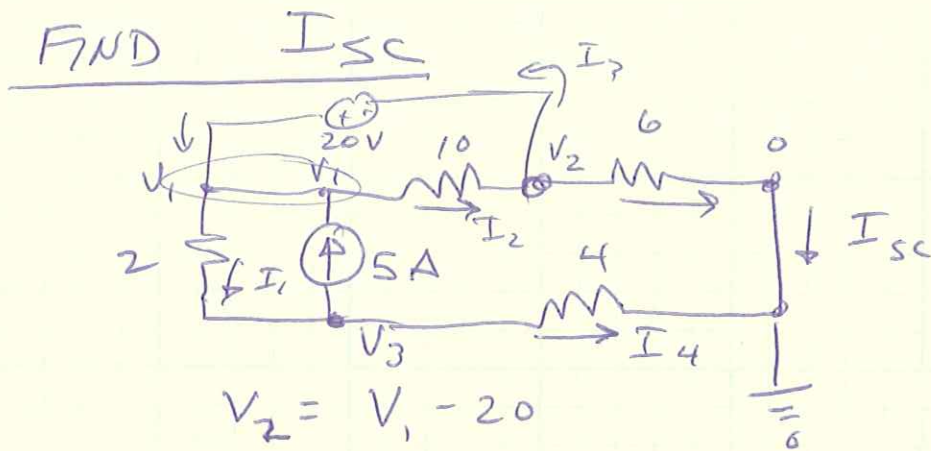


$$I_{sc} = \frac{V_2}{6} = \frac{V_1 - 20}{6}$$

KCL
 V_1 $\frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{10} =$



KCL @ V_2 $I_2 = I_3 + I_{sc}$

I_{sc}

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

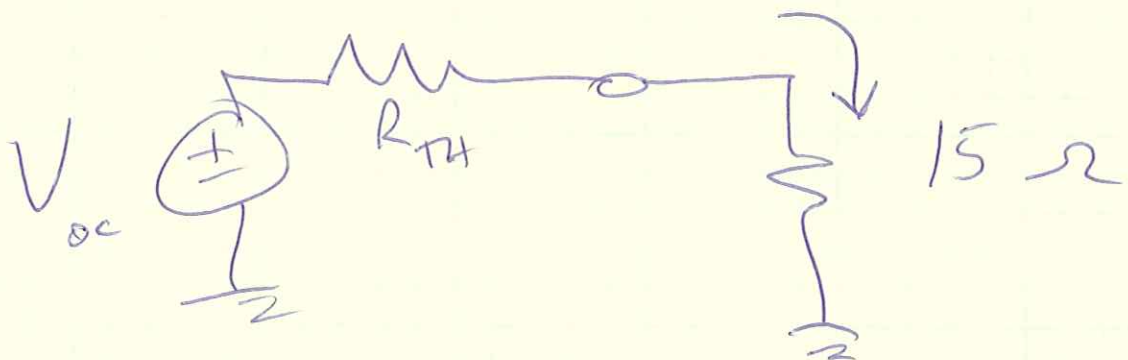


FINDING T.E.C

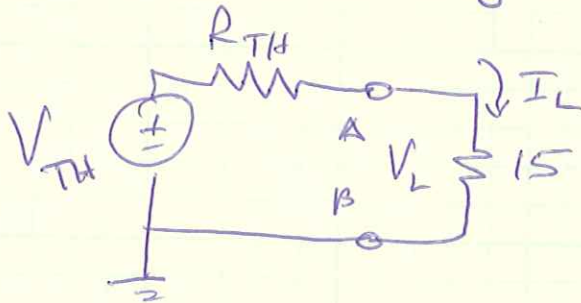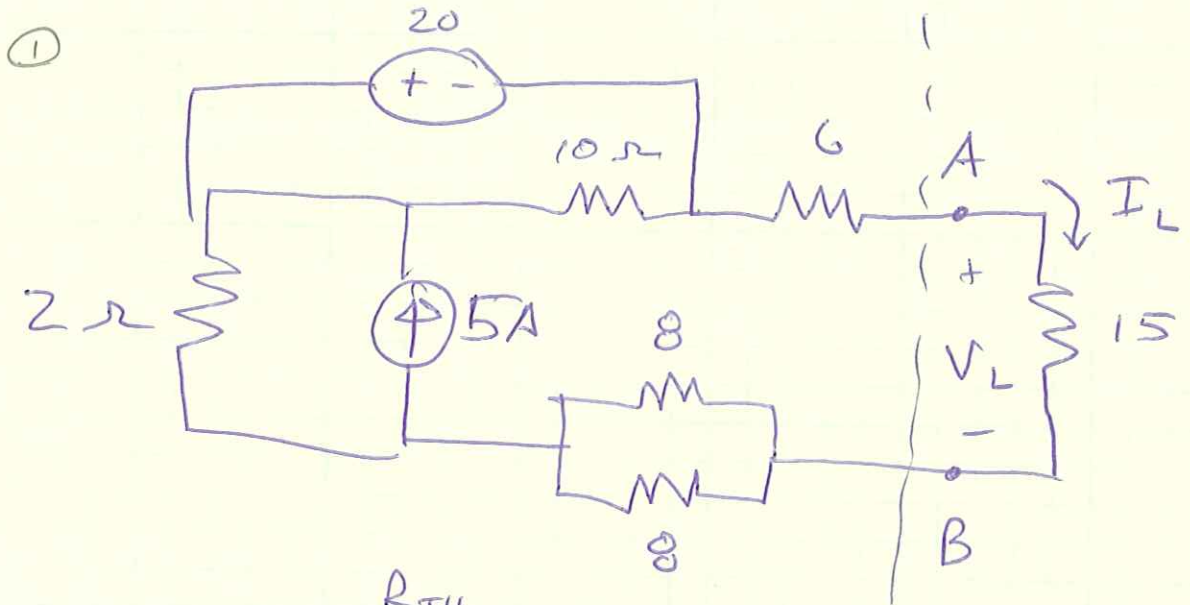


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$V_L = 15 I_L$$

DIODES

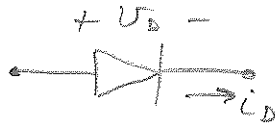

FORWARD

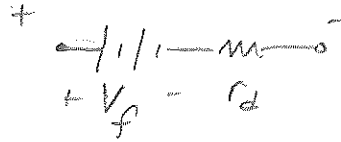


$$V_D = V_f + i_D r_d$$

$$r_d = \frac{25 \text{ mV}}{I_D'}$$

REVERSE



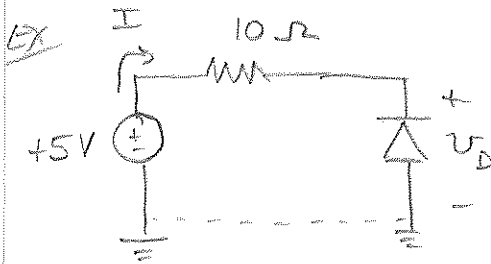$I_D' \equiv$ APPROXIMATE CURRENT SHORT CIRCUIT



FIND : I , V_D , i_D

GIVEN : $V_f = 0.7 \text{ V}$

WHAT DO WE KNOW?

$$i_D = I$$


DIODE REVERSE



NO PATH $I = i_D = 0$

$$V_D = 5 \text{ V}$$



EX

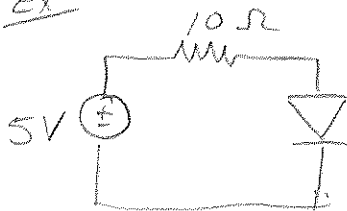

DIODE FWD.

$$I_D' = \frac{5 - 0}{10} = 0.5 \text{ A}$$
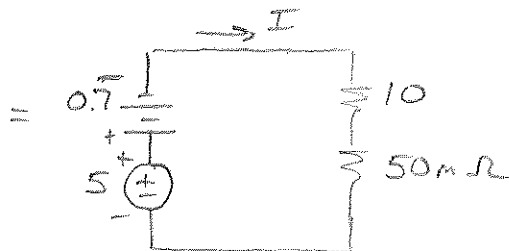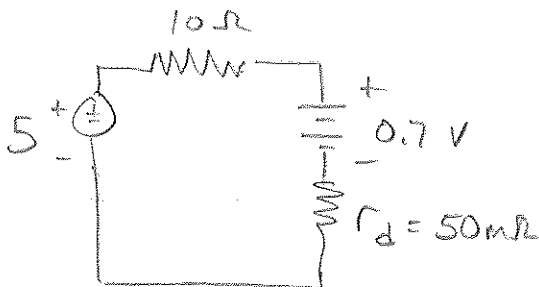
$$r_d = \frac{25 \text{ mV}}{0.5 \text{ A}} = 50 \text{ m}\Omega$$




$$4.3 = I (10.05)$$

$$I = .428 \text{ A}$$

$$V_D = .7 + .428(50)$$

$$= .721 \text{ V}$$


IDEAL OP-AMPS

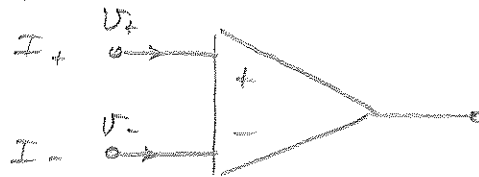

$$A_o = \infty$$

$$I_+ = I_- = 0$$

$$V_+ = V_-$$

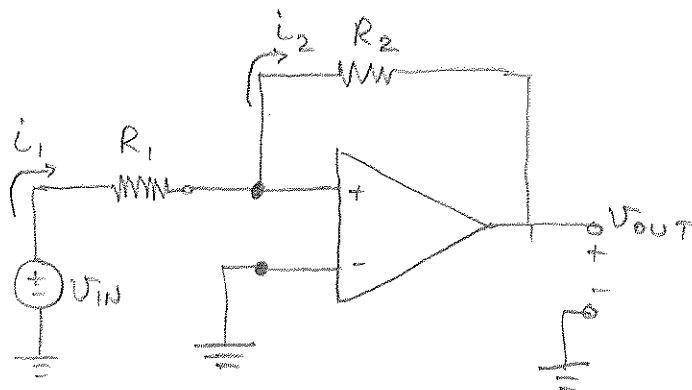

$$\text{FIND: } \frac{V_{OUT}}{V_{IN}}$$

$$I_1, I_2 \text{ IF } V_{IN} = 5V$$

$$R_1 = 1K\Omega$$

$$R_2 = 10K\Omega$$

ASSUME IDEAL OP-AMP

WHAT DO WE KNOW?

$$\text{I) } V_- = V_+ \quad I_+ = I_- = 0$$

$$\text{II) } V_- = 0 \text{ (CONNECTED TO GROUND)} \quad V_+ = 0$$

$$\text{III) } I_1 = \frac{V_{IN} - V_+}{R_1} \quad \text{OHMS LAW} \quad = \underline{\underline{5mA}}$$

$$\text{IV) } \begin{array}{c} \xrightarrow{I_1} \uparrow I_2 \\ \text{Node } V_+ \end{array} \quad \text{KCL @ NODE } V_+$$

$$I_1 = I_2 + I_+$$

$$I_1 = I_2 = 5mA$$


$$\sum I_{IN} = \sum I_{OUT}$$

$$\text{V) } \begin{array}{c} R_2 \\ \xrightarrow{I_2} \\ V_+ \quad V_{OUT} \end{array} \quad I_2 = \frac{V_+ - V_{OUT}}{R_2} = \frac{-V_{OUT}}{R_2} = I_2$$

$$I_1 = I_2$$

$$\frac{-V_{OUT}}{R_2} = \frac{V_{IN}}{R_1}$$
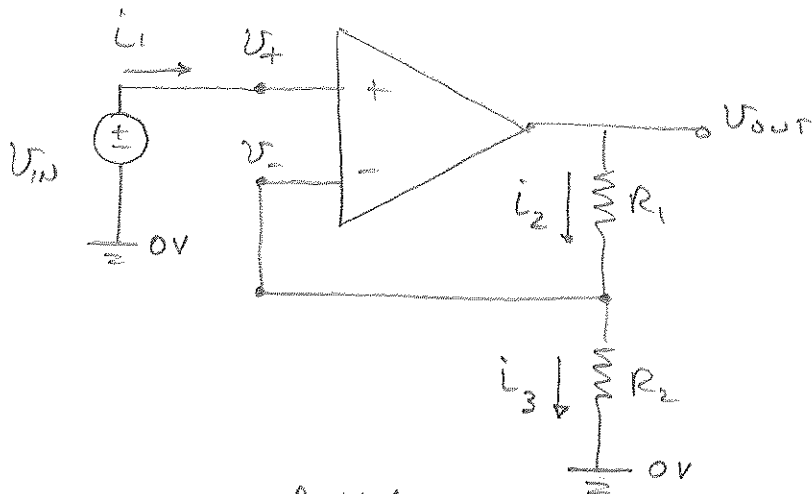
$$\frac{V_{OUT}}{V_{IN}} = \frac{-R_2}{R_1}$$



ASSUME IDEAL OP-AMP


FIND $\frac{V_{OUT}}{V_{IN}}$ I_1 , I_2 , I_3 IF $V_{IN} = 5V$ $R_1 = 5k\Omega$
 $R_2 = 1k\Omega$

WHAT DO WE KNOW?

I) $V_+ = V_-$ $I_+ = I_- = 0$

II) $V_+ = V_{IN}$ $I_1 = I_+$ $I_2 = I_3$ (KCL)
 $V_- = V_+ = V_{IN}$

III)

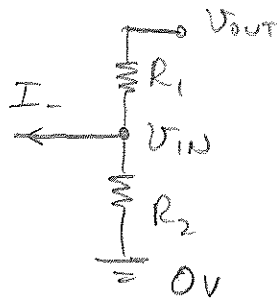

R_1 AND R_2 SHARE CURRENT

$$I_2 = I_3$$

$$I_3 = \frac{V_{IN} - 0}{R_2}$$

$$I_2 = \frac{V_{OUT} - V_{IN}}{R_1}$$


$$I_3 = I_2$$

$$\frac{V_{IN}}{R_2} = \frac{V_{OUT} - V_{IN}}{R_1}$$

$$\frac{R_1}{R_2} V_{IN} + V_{IN} = V_{OUT}$$

$$\frac{R_1}{R_2} + 1 = \boxed{\frac{V_{OUT}}{V_{IN}} = \frac{R_1 + R_2}{R_1}}$$


VOLTAGE DIVIDER

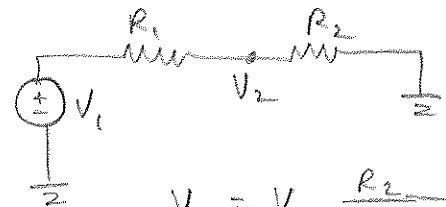

$$V_2 = V_1 \frac{R_2}{R_1 + R_2}$$

$$V_2 = V_{IN}$$

$$V_1 = V_{OUT}$$

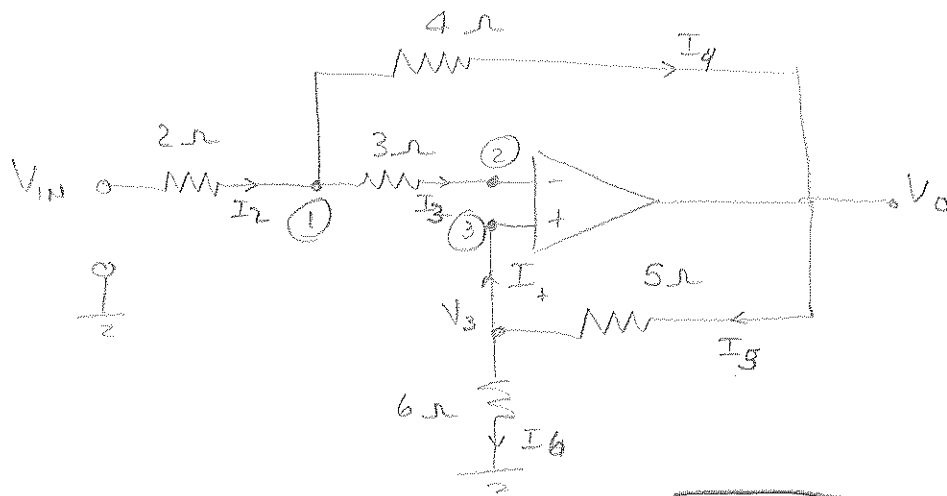

FIND $\frac{V_o}{V_{IN}}$

NODE 3

$$I_5 = I_6$$

$$\frac{V_o - V_3}{5} = \frac{V_3 - 0}{6}$$

$$6V_o - 6V_3 = 5V_3$$

$$6V_o = 11V_3$$

$$V_3 = \frac{6}{11} V_o$$

ALSO BY
VOLTAGE
DIVISION

USING IDEAL PROPERTIES:

$$I_3 = 0 \quad I_2 = I_4$$

$$I_4 = 0 \quad I_5 = I_6$$

$$V_3 = V_1$$

$$V_3 = V_o \left(\frac{6}{5+6} \right) = V_1$$

NODE 1

$$\frac{V_{IN} - V_1}{2} = \frac{V_1 - V_o}{4} \rightarrow \frac{V_{IN} - \frac{6}{11} V_o}{2} = \frac{\frac{6}{11} V_o - V_o}{4}$$

$$2V_{IN} - \frac{12}{11} V_o = -\frac{5}{11} V_o$$

$$2V_{IN} = \frac{7}{11} V_o$$

$$\frac{V_o}{V_{IN}} = \frac{22}{7}$$

Time Domain

Phasor

R \longrightarrow

R

$$v(t) = L \frac{di(t)}{dt}$$

L \longrightarrow

$$j\omega L$$

$$= Z_L$$

$$\vec{V} = L j\omega \vec{I}$$

$$\cancel{V_{\text{phasor}}} = L j\omega I_{\text{phasor}} \quad C \longrightarrow$$


$$Z_C = \frac{1}{j\omega C}$$

$$V = j\omega I_m L$$

$$V = \underbrace{(j\omega L)}_{Z_L} I_m$$

AC CIRCUITS


CAPACITORS

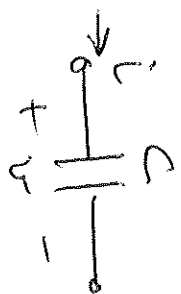

$$i(t) = C \frac{dv(t)}{dt}$$



INDUCTORS

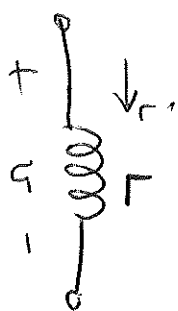

$$v(t) = L \frac{di(t)}{dt}$$




RESISTORS



$$v = i R$$

$$v(t) = i(t) R$$

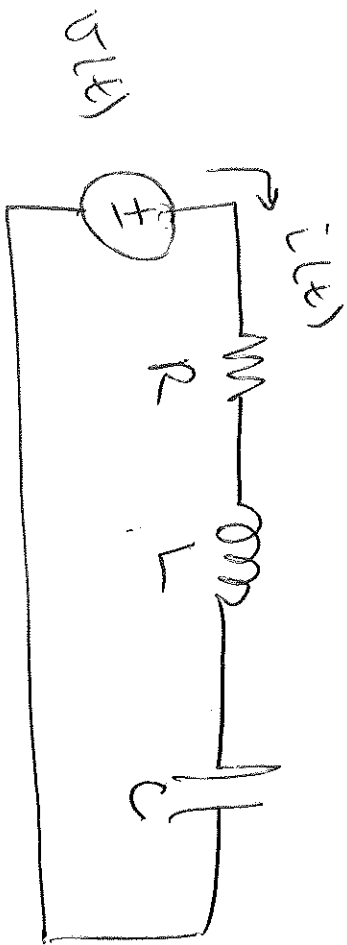

$$v(t) = 10 \cos(\omega t + \theta)$$


$$\vec{V} = 10 e^{j(\omega t + \theta)}$$

PHASOR

$$v(t) = \text{Re}[\vec{V}]$$

$$i = I_m e^{j(\omega t + \theta)}$$

$$I_m$$

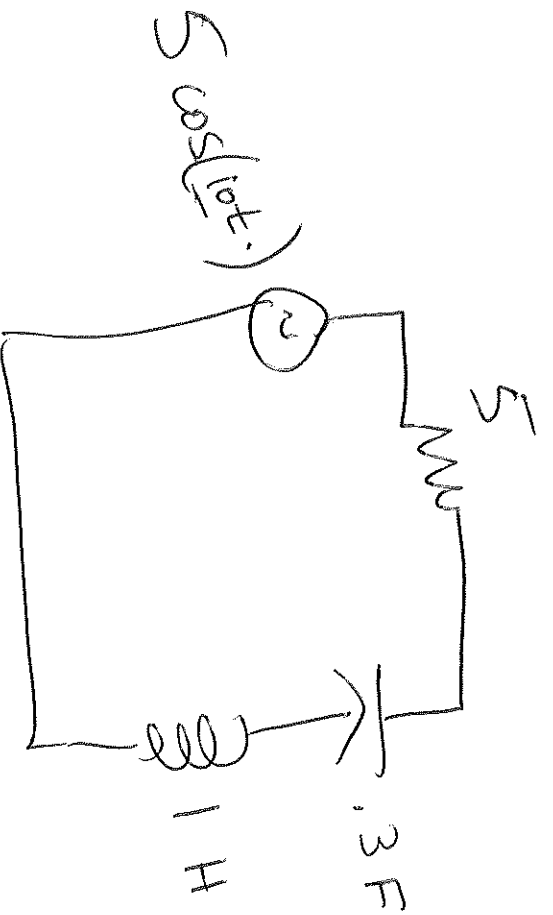

$$\underline{\text{Find } i(t)}$$

$$V = I Z_T$$

$$\frac{1}{j10(.3)} = -\frac{j}{3}$$


$$I = \frac{5 \angle 0^\circ}{5 + \frac{-j}{3} + j10}$$

$$= \frac{5 \angle 0^\circ}{5 + j9.67}$$


$$= \frac{5 \angle 0^\circ}{10.89 \angle 62.6^\circ}$$

$$I = .459 \angle -62.6^\circ$$
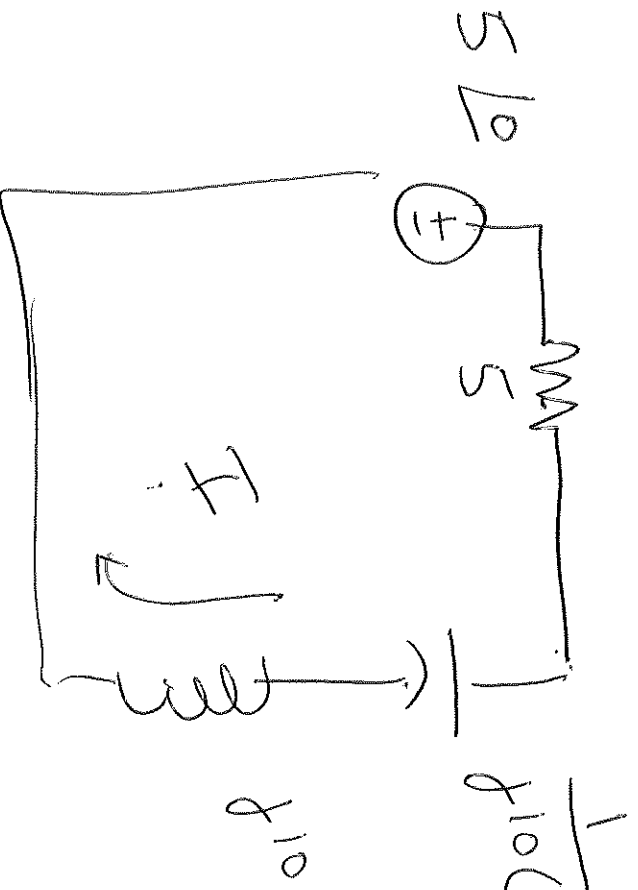
$$i(t) = .459 \cos(10t - 62.6^\circ) \text{ A}$$



TRANSIENT CIRCUITS

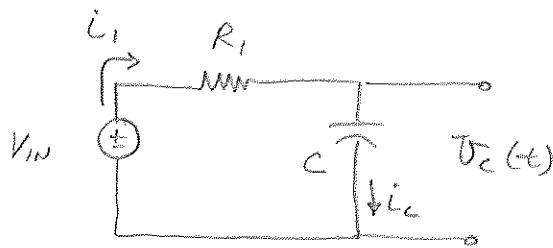

FIND $V_C(t)$

$i_1(t)$

WHAT DO WE KNOW?

$$i_C = C \frac{dV_C(t)}{dt}$$

V-I LAW OF CAPACITORS

$$i_C = i_1$$

KCL

$$i_1 = \frac{V_{IN} - V_C(t)}{R_1}$$

OHMS LAW

$$\text{I) } \frac{V_{IN} - V_C(t)}{R_1} = C \frac{dV_C(t)}{dt}$$

$$\frac{dV_C(t)}{dt} + \frac{1}{RC} V_C(t) = \frac{1}{RC} V_{IN}(t)$$

FIRST ORDER
CONSTANT COEFF. DIFFEQ

$$\text{IF } v_{in}(t) = A e^{3t}$$

$$v_c(t) = K e^{st}$$

HOMOGENEOUS SOLN

$$\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = 0$$

$$K s e^{st} + \frac{K}{RC} e^{st} = 0$$

$$K e^{st} \left(s + \frac{1}{RC} \right) = 0 \quad \boxed{s = -\frac{1}{RC}} \quad v_c(t) = K e^{-t/RC}$$

PARTICULAR SOLUTION

$$v_c(t) = V_c e^{3t}$$

$$3 V_c e^{3t} + \frac{V_c}{RC} e^{3t} = A e^{3t}$$

$$3 V_c + \frac{V_c}{RC} = A$$

$$V_c = \frac{A}{\left(3 + \frac{1}{RC}\right)}$$

$$v_c(t) = \frac{A}{\left(3 + \frac{1}{RC}\right)} e^{3t}$$

TOTAL

$$v_c(t) = K e^{-t/RC} + \frac{A}{\left(3 + \frac{1}{RC}\right)} e^{3t}, \quad t > 0$$

ASSUME $v_c(t) = 0$ FOR $t < 0$ (INITIAL CONDITIONS)

$$0 = K + \frac{A}{\left(3 + \frac{1}{RC}\right)}$$

$$K = \frac{-A}{\left(3 + \frac{1}{RC}\right)}$$

$$v_c(t) = \frac{A}{\left(3 + \frac{1}{RC}\right)} \left[e^{3t} - e^{-t/RC} \right], \quad t > 0$$

AS $t \rightarrow \infty$ STEADY STATE $v_c(t) \rightarrow \frac{A}{\left(3 + \frac{1}{RC}\right)} e^{3t}$

~~$v_c(t) =$~~

$$v_c(t) = \frac{A}{3 + \frac{1}{RC}} \left[e^{3t} - e^{-\frac{t}{RC}} \right], \quad t > 0$$

ex

$$R = 1 \text{ k}\Omega$$


$$C = 1 \mu\text{F}$$

$$v_{in}(t) = 5e^{3t}$$

Steady State Expression

as $t \rightarrow \infty$
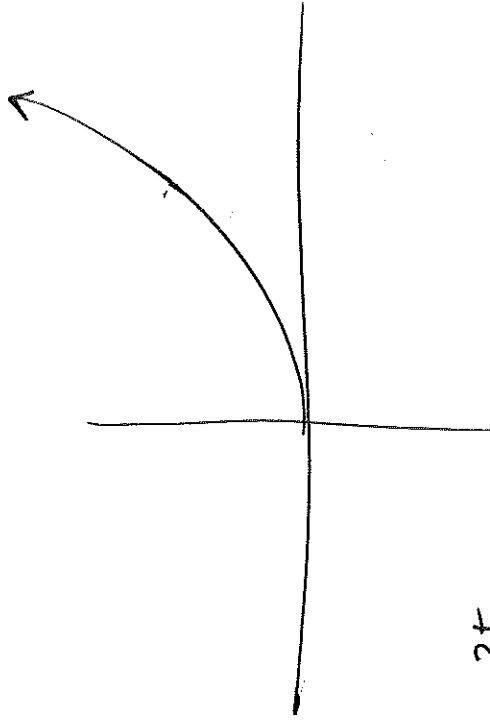
$$v_c(t) \Rightarrow \left[\frac{A}{3 + \frac{1}{RC}} \right] e^{3t}$$



$$\frac{d x(t)}{dt} + a x(t) = f(t)$$

IF $x_p(t)$ IS A SOLN, AND $x_c(t)$ IS A SOLN
TO THE HOMOGENEOUS EQN:

$$\frac{d x(t)}{dt} + a x(t) = 0$$

Then

$$x(t) = x_p(t) + x_c(t)$$

LET $f(t) = A$ constant

$$\frac{d x_p(t)}{dt} + a x_p(t) = A$$

$$x_p(t) = K_1$$

$$\frac{d x_c(t)}{dt} + a x_c(t) = 0$$

$$x_p(t) = K_1 = \frac{A}{a}$$

$$x_c(t) = K_2 e^{-at}$$

$$x(t) = K_1 + K_2 e^{-at}$$

USING LAPLACE TRANSFORMS

$$V_c(t) + CR \frac{dV_c}{dt} = 0$$

$$V(0^-) = V_s$$

$$V(s) + CR(sV(s) - V(0^-)) = 0$$

$$V(s)(1 + CRS) - CRV(0^-) = 0$$

$$V(s) = \frac{CR V_s}{1 + CRS} = \frac{V_s}{\frac{1}{RC} + s}$$

$$V(t) = V_s e^{-\frac{1}{RC}t}$$

$$\frac{1}{s+a} \leftrightarrow e^{-at}$$

$$\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = \frac{V_s}{RC}$$

$$sV(s) + \frac{V(s)}{RC} = \frac{V_s}{sRC}$$

$$V(s) \left(s + \frac{1}{RC} \right) = \frac{V_s}{s} = \frac{k_1}{s} + \frac{k_2}{s + \frac{1}{RC}}$$


$$\frac{\frac{V_s}{RC}}{\frac{1}{RC}} = \boxed{k_1 = V_s}$$

$$\frac{\frac{V_s}{RC}}{s} \bigg|_{s = -\frac{1}{RC}} = \boxed{k_2 = -V_s}$$

$$V(t) = V_s - V_s e^{-\frac{t}{RC}}$$

AC SS CRT ANALYSIS INIT. COND = 0

SINUSOIDAL RESPONSE

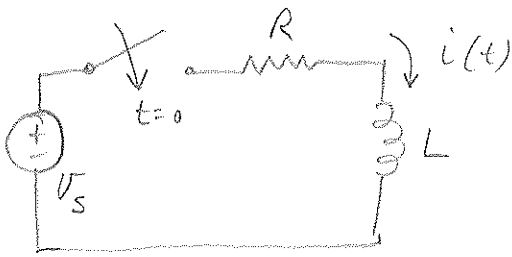

$$V_s(t) = V_m \cos(\omega t + \phi_v)$$

$$L \frac{di(t)}{dt} + Ri(t) = V_m \cos(\omega t + \phi_v)$$

$$i(t) = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi_v - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi_v - \theta)$$

↑
Homogeneous
(transient)

as $t \rightarrow \infty$
term $\rightarrow 0$

↑
Particular
(sinusoidal)
Steady state

$$i_{ss}(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi_v - \theta)$$

$$I_{max} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\text{Let } \phi_v - \theta = \theta_i$$

$$i_{ss}(t) = I_m \cos(\omega t + \theta_i)$$

Phasors

$$V(t) = V_m \cos(\omega t + \phi_v) \rightarrow \underline{V} = V_m \angle \phi_v$$

$$i(t) = I_m \cos(\omega t + \theta_i) \rightarrow \underline{I} = I_m \angle \theta_i$$

AC CIRCUIT ANALYSIS - STEADY STATE ANALYSIS


CONVERT TO PHASOR DOMAIN

$$v(t) = A \cos(\omega t + \theta) = \text{Re} [A e^{j(\omega t + \theta)}]$$


ALSO WRITTEN AS A PHASOR $\underline{V} = A \angle \theta$

CONVERT COMPONENTS

<u>TIME DOMAIN</u>		<u>PHASOR</u>
R	\rightarrow	R
L	\rightarrow	$j\omega L$
C	\rightarrow	$\frac{1}{j\omega C}$

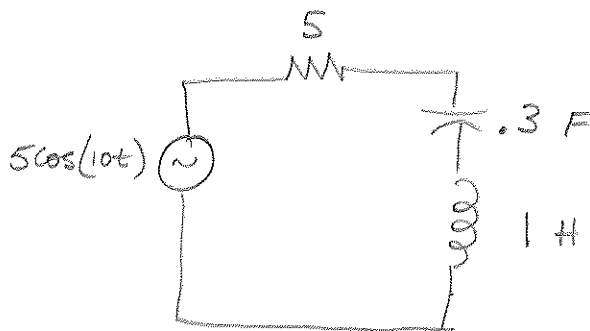

\rightarrow

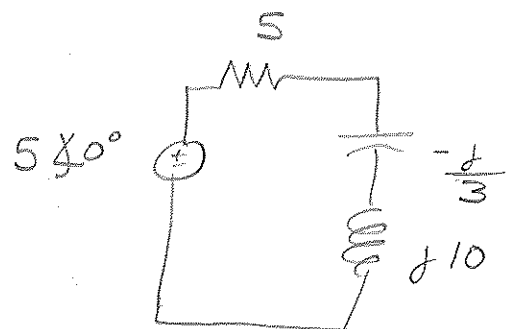

$$I = \frac{5 \angle 0^\circ}{5 - \frac{j}{3} + j10}$$

$$I = \frac{5 \angle 0^\circ}{5 + j(10 - \frac{1}{3})}$$

PHASOR NOTATION - A COMPLEX NUMBER THAT
CARRIES AMPLITUDE AND PHASE ANGLE OF A
SINUSOIDAL FUNCTION

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\operatorname{Re}\{e^{j\theta}\} = \cos\theta$$

$$\operatorname{Im}\{e^{j\theta}\} = \sin\theta$$

$$v(t) = V_m \cos(\omega t + \phi)$$


$$= V_m \operatorname{Re}\{e^{j(\omega t + \phi)}\} = V_m \operatorname{Re}\{e^{j\omega t} e^{j\phi}\}$$

$$= \operatorname{Re}\{\underbrace{V_m e^{j\phi}} e^{j\omega t}\}$$

PHASOR OF $v(t)$ \vec{V}

$$\vec{V} = V_m e^{j\phi} = V_m \cos\phi + j V_m \sin\phi = V_m \angle \phi$$

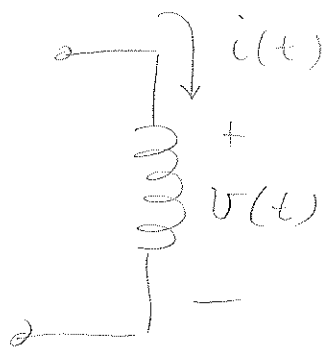Ex $\vec{V} = 100 \angle -26^\circ \rightarrow v(t) = 100 \cos(\omega t - 26^\circ)$



$$v(t) = L \frac{d i(t)}{dt}$$

$$\begin{aligned} i(t) &= I_M \cos(\omega t + \theta_i) \\ v(t) &= V_M \cos(\omega t + \theta_v) \end{aligned}$$

$$V = V_M e^{j\theta_v} e^{j\omega t}$$

$$i(t) = \text{Re} \{ \vec{I} \}$$


$$I = \underbrace{I_M e^{j\theta_i}}_{\vec{I}} e^{j\omega t}$$

$$V_M e^{j\theta_v} e^{j\omega t} = L I_M e^{j\theta_i} j\omega e^{j\omega t}$$

$$V_M e^{j\theta_v} = I_M e^{j\theta_i} j\omega L$$

$$\vec{V} = \underbrace{\vec{I} j\omega L}_{Z_L}$$

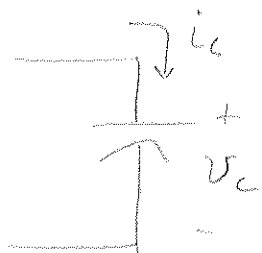Z_L INDUCTOR IMPEDANCE IS NOW
COMPLEX AND FREQUENCY DEPENDENT.



$$i_c = C \frac{dv_c(t)}{dt}$$

$$I_M e^{j\theta_i} e^{j\omega t} = C V_M e^{j\theta_v} j\omega e^{j\omega t}$$

$$I_M e^{j\theta_i} = j\omega C V_M e^{j\theta_v}$$

$$V_M e^{j\theta_v} = \frac{I_M e^{j\theta_i}}{j\omega C}$$

$$\vec{V} = \vec{I} Z_C$$

$$Z_C = \frac{1}{j\omega C}$$

$$I = \frac{5 \angle 0^\circ}{5 + j9.67} = \frac{5 \angle 0^\circ}{10.89 \angle 62.6^\circ} = 0.459 \angle -62.6^\circ$$

$$i(t) = 0.459 \cos(10t - 62.6^\circ)$$

SUMMARY OF COMPLEX NUMBERS

$$x + jy = r e^{j\theta}$$

$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \theta$$

$$y = r \sin \theta$$

$$A e^{jx} = A(\cos x + j \sin x)$$

$$\operatorname{Re}\{e^{jx}\} = \cos x$$

$$\frac{1}{e^{j\theta}} = e^{-j\theta} \quad \text{or} \quad \frac{1}{5 \angle 30^\circ} = 0.2 \angle -30^\circ$$


COMPLEX IMPEDANCE

$$Z = R + jX$$


↑
Real

↑
reactive

$$V = I Z$$

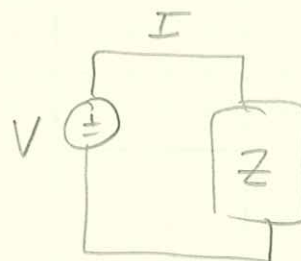

MAGNETIC FIELDS

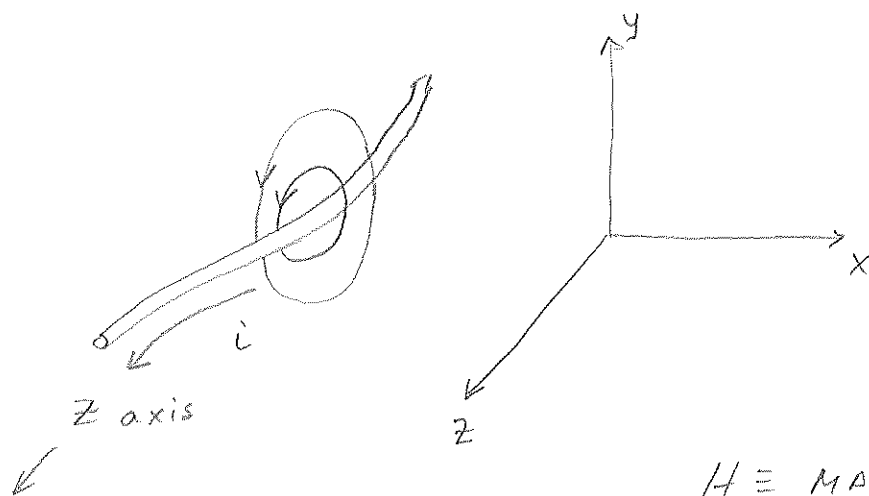

$\curvearrowright \Phi_{pos}$

$$H = \frac{B}{\mu} = \frac{I \vec{a}_{\phi}}{2\pi r}$$

$H \equiv$ MAG FIELD STRENGTH (A/m)

$B \equiv$ MAG FLUX DENSITY (TESLA)


$\vec{a}_{\phi} \equiv$ unit vector in pos ϕ direction
in cylindrical coordinates

$I =$ current

$\mu =$ permeability of medium
(air, iron core)


air $4\pi \times 10^{-7}$ H/m

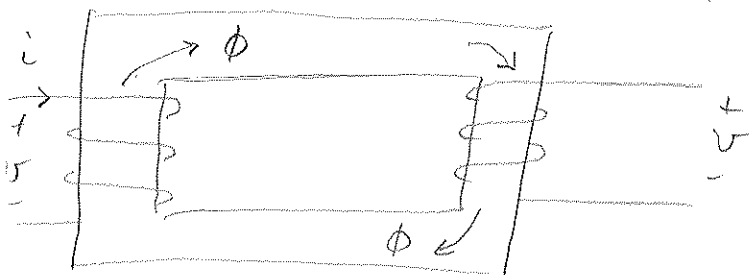MAGNETIC
 Φ FLUX ENCLOSED BY N TURNS OF WIRE




$$V = -N \frac{d\phi}{dt} \quad \text{INDUCED VOLTAGE}$$
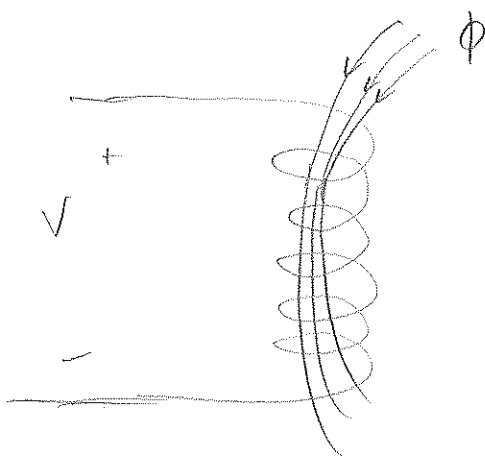
$$\phi = \oint_S B \cdot dS = \text{TOTAL FLUX IN A VOLUME}$$



TOTAL VOLUME OF MATERIAL DENSITY IS WEIGHT
TOTAL VOLUME OF B IS ϕ

THE IDEAL TRANSFORMER

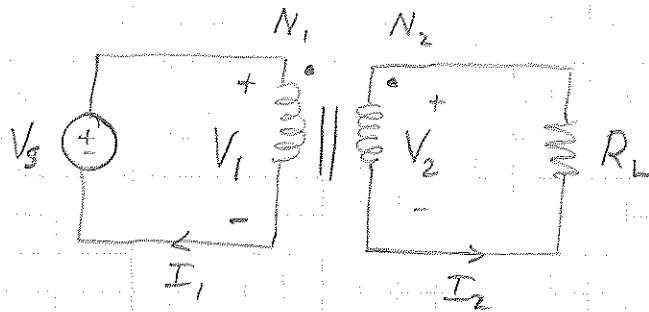


coil 1 $P_1 = V_1 I_1$ ABSORBED

coil 2 $P_2 = V_2 I_2$ supplied.



$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$N_1 I_1 = -N_2 I_2$$


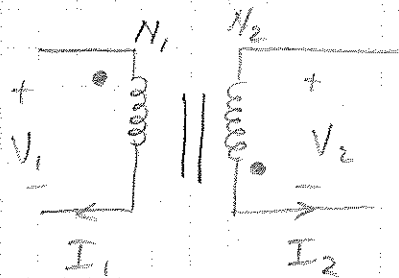


$$a = \frac{N_2}{N_1}$$

$$\frac{V_1}{N_1} = -\frac{V_2}{N_2}$$

$$N_1 I_1 = N_2 I_2$$
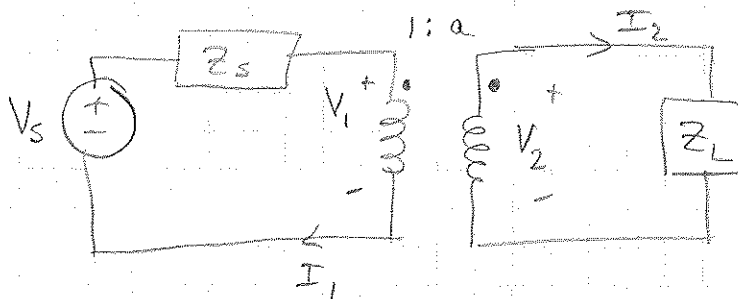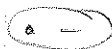
$$\rightarrow I_1 \quad \dots \quad \rightarrow I_2$$




$$V_2 = a V_1$$

$$I_2 = \frac{I_1}{a}$$

$$Z_{in} = \frac{Z_L}{a^2}$$

IDEAL TRANSFORMERS

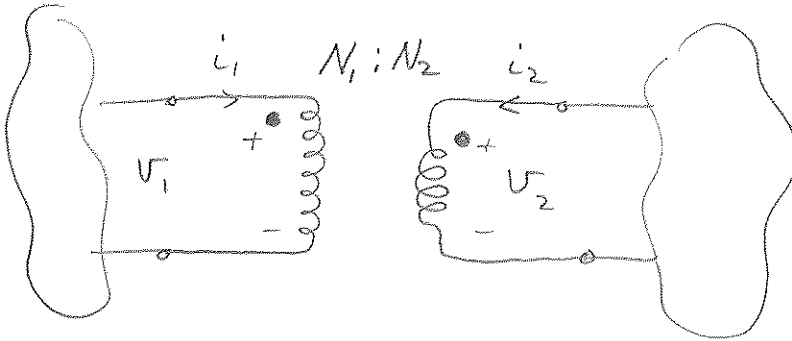

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

$$V_1 i_1 + V_2 i_2 = 0$$

NO POWER LOST IN AN
IDEAL XFORMER


$$\eta = \frac{N_2}{N_1} \quad \text{:= turns ratio}$$

$$V_1 = \frac{V_2}{\eta}$$

$$I_1 = \eta I_2$$

$$Z_1 = \frac{Z_L}{\eta^2}$$


IDEAL TRANSFORMERS

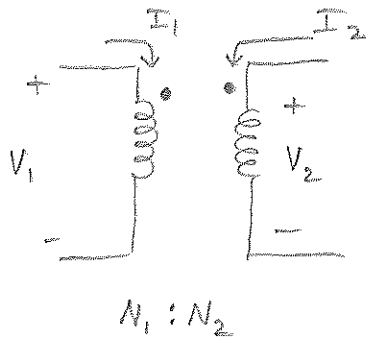

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{I_1}{I_2} = -\frac{N_2}{N_1}$$

EX

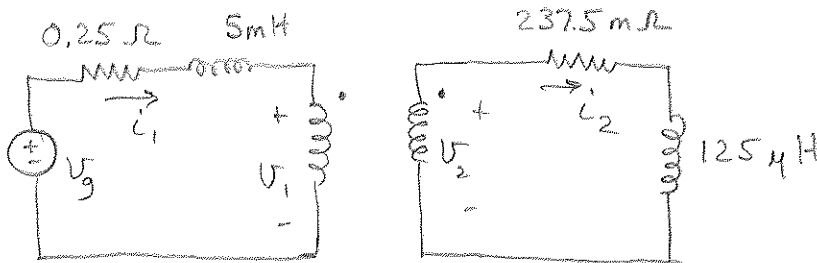

$$V_g = 2500 \cos 400t$$

FIND STEADY STATE I_1, V_1, I_2, V_2

$$V_g \Rightarrow \vec{V}_g = 2500 \angle 0^\circ$$

$$L_1 = 5\text{mH} \quad Z_{L_1} = j(5\text{mH})(400) = j2$$

$$L_2 = 125\mu\text{H} \quad Z_{L_2} = j(125\mu\text{H})(400) = j0.05$$

$$\frac{V_g - V_1}{.25 + j2} = I_1$$

$$\frac{I_1}{-I_2} = -\frac{N_2}{N_1}$$

$$\frac{I_1}{I_2} = \frac{1}{10}$$

$$10 I_1 = I_2$$

$$V_2 = I_2 (.2375 + j0.05)$$

$$V_2 = \frac{V_1}{10}$$

$$V_1 = 10 I_2 (.2375 + j0.05)$$

$$V_1 = (10)(10) I_1 (.2375 + j0.05)$$

$$V_1 = I_1 (23.75 + j5)$$

*

STEADY STATE \Rightarrow PHASORS
DROP FREQUENCY

$$v(t) = V \cos(\omega t + \theta)$$

$$\vec{V} = V \angle \theta$$

$$Z_L = j\omega L \quad Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

$$V_G = I_1 (.25 + j2) + V_1$$

$$= I_1 (.25 + j2) + I_1 (23.75 + j5)$$

$$V_G = I_1 (24 + j7)$$

$$\frac{2500 \angle 0^\circ}{25 \angle 16.26^\circ} = I_1$$

$$I_1 = 100 \angle -16.26^\circ \text{ A}$$

$$25 \angle 16.26^\circ$$

$$i_1(t) = 100 \cos(400t - 16.26^\circ) \text{ A}$$


$$I_2 = 10 I_1 = 1000 \cos(400t - 16.26^\circ) \text{ A} = i_2(t)$$

$$V_1 = I_1 (23.75 + j5) = (100 \angle -16.26^\circ) (24.27 \angle 11.89^\circ) \\ = 2427 \angle -4.37^\circ$$

$$v_1(t) = 2427 \cos(400t - 4.37^\circ) \text{ V}$$

$$V_2 = \frac{V_1}{10} = 242.7 \angle -4.37^\circ$$
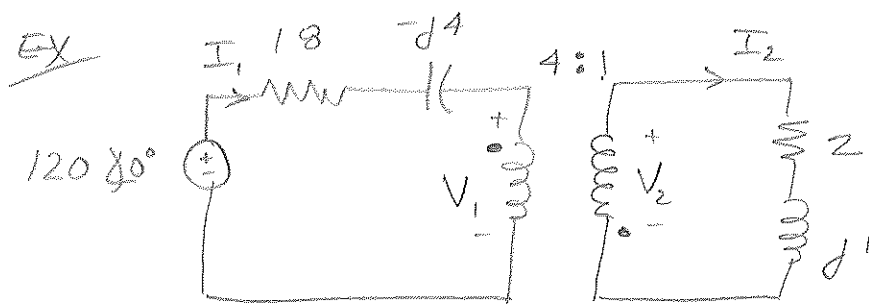
$$v_2(t) = 242.7 \cos(400t - 4.37^\circ) \text{ V}$$




$$V_1 = -\frac{V_2}{n}$$

$$I_1 = -n I_2$$

$$n = \frac{1}{4}$$

$$Z_1 = \frac{Z_L}{n^2} = 4^2 Z_L$$

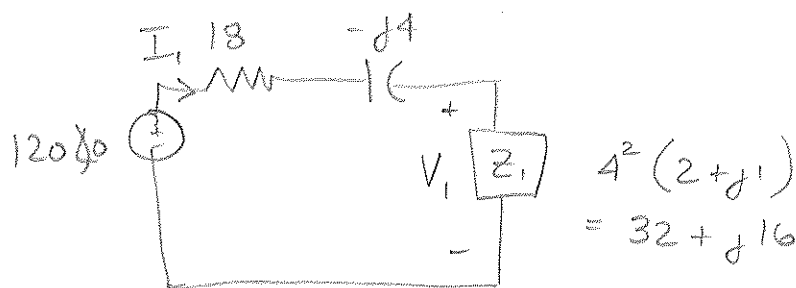

$$I_1 = \frac{120 \angle 0^\circ}{18 - j4 + 32 + j16} = 2.33 \angle -13.5^\circ$$


$$V_1 = I_1 Z_1 = (2.33 \angle -13.5^\circ)(32 + j16) = 83.49 \angle 13.07^\circ$$

$$V_2 = -V_1 n = \frac{1}{4} 83.49 \angle 13.07^\circ = 20.87 \angle 13.07^\circ$$

$$I_2 = -\frac{I_1}{n} = 4(2.33 \angle 13.5^\circ) = 9.33 \angle 136.5^\circ$$

POWER


$$p = v i$$

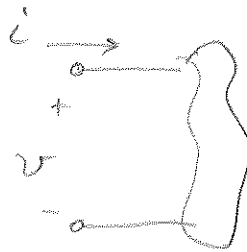

PASSIVE SIGN
CONVENTION

POSITIVE POWER
(absorbed)


DC

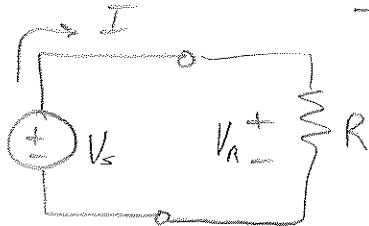

$$P_s = -VI$$

$$P_R = V_R I = I^2 R = \frac{V_R^2}{R}$$

$$V_R = IR$$

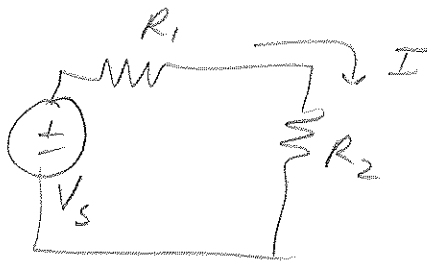

$$P_{R_2} = V_{R_2} I = \frac{V_{R_2}^2}{R_2}$$

AC

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

USING AN ARBITRARY REFERENCE TIME WE CAN WRITE

$$i(t) = I_m \cos \omega t$$

$$v(t) = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$p = v(t) i(t) = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos \omega t$$

USING: $\cos \alpha \cos \beta = \frac{1}{2} \cos(\alpha - \beta) + \frac{1}{2} \cos(\alpha + \beta)$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$

AVERAGE (REAL) POWER $P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$

REACTIVE POWER $Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$

$$p(t) = P + P \cos 2\omega t - Q \sin 2\omega t$$

P IS NOT TIME DEPENDENT. (CONSTANT, LIKE DC)

$$P = (V_{rms})(I_{rms})(pf)$$

V_{rms} } DC EQUIVALENT ROOT MEAN SQUARED
 I_{rms} }

FOR SINUSOIDAL $v(t), i(t)$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

pf: power factor $\cos(\theta_v - \theta_i)$

$$-1 < pf < 1$$

$$pf > 0$$


lagging pf

CURRENT LAGS VOLTAGE

$$pf < 0$$

leading pf

CURRENT LEADS VOLTAGE.

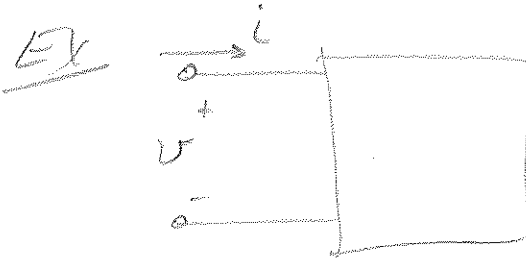

$$v = 100 \cos(\omega t + 15^\circ) \text{ V}$$

$$i = 4 \sin(\omega t - 15^\circ) \text{ A}$$

FIND AVG POWER AND REACTIVE POWER AT TERMINALS


$$V = 100 \angle 15^\circ$$

$$I = 4 \angle -15^\circ - 90^\circ = 4 \angle -105^\circ$$

$$P = \frac{100(4)}{2} \cos(15^\circ + 105^\circ) = 200(-.5) = -100 \text{ W}$$

SUPPLIED!
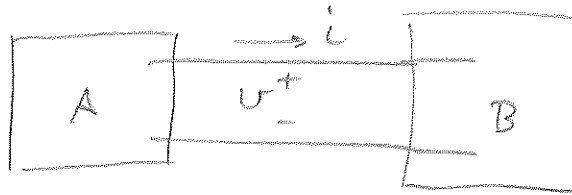
$$Q = \frac{100(4)}{2} \sin(120^\circ) = +173.2 \text{ VAR}$$



a)

$$v = 100 \cos(\omega t - 45^\circ)$$

$$i = 20 \cos(\omega t + 15^\circ)$$

$$P = \frac{100(20)}{2} \cos(-45 - 15)$$

$$= 100(.5) = +50 \text{ W}$$

POWER FROM A to B

$$Q = \frac{100(20)}{2} \sin(-60)$$

$$= -866.03 \text{ VAR}$$

DELIVERING (MAGNETIZING) FROM B to A
VARs

$$p(t) = 50 + 50 \cos 2\omega t + 866.03 \sin 2\omega t$$



ENERGY BEING STORED IN MAGNETIC FIELDS
ASSOCIATED WITH INDUCTIVE ELEMENTS.

Complex Power

AC

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

INSTANTANEOUS POWER $p(t) = v(t) i(t) = I_m V_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$

$$p(t) = \frac{V_m I_m}{2} \left[\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i) \right]$$

↑
TIME IND.

↑
TIME DEP.

AVERAGE POWER

$$P_{av} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m \angle \theta_v}{\sqrt{2}} \frac{I_m \angle \theta_i}{\sqrt{2}}$$

$$pf \equiv \text{power factor} = \cos(\theta_v - \theta_i) = V_{rms} I_{rms} (pf)$$


DIFFERENCE IN PHASE ANGLE
OF V and I

SINUSOIDAL R.M.S.

$$V_{rms} I_{rms} \equiv \text{APPARENT POWER}$$

$$1 \leq \cos(\theta_v - \theta_i) \leq 1 \quad \begin{array}{ll} 0 < pf < 1 & \text{lagging pf} \\ -1 < pf < 0 & \text{leading pf} \end{array}$$

EX

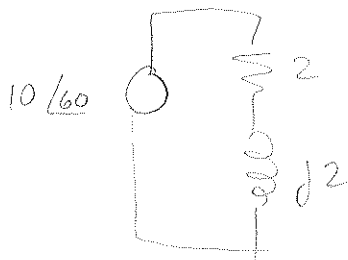

FIND P_{ave} , pf

$$V = 10 \angle 60^\circ$$

$$I = \frac{10 \angle 60^\circ}{2 + j2} = 3.53 \angle 15^\circ$$

$$P_{ave} = \frac{10(3.53)}{2} \cos(60 - 15) = 12.48 \text{ Watts}$$

$$pf = \cos(45^\circ) = .707 \text{ lagging (INDUCTIVE LOAD)}$$


COMPLEX POWER

$$S = P + jQ$$

$$P = \operatorname{Re}\{S\} \quad \text{WATTS}$$

$$Q = \operatorname{Im}\{S\} \quad \text{VARs}$$

$$S \quad \text{VOLT-AMPS}$$

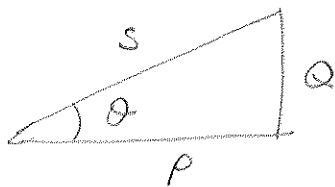

$$\theta = \theta_v - \theta_i$$

$$|S| = \sqrt{P^2 + Q^2} \quad \tan \theta = \frac{Q}{P}$$

$$|S| \equiv \text{APPARENT POWER} \quad \text{VOLT-AMPS}$$

EX LOAD @ 240 V_{rms} ABSORBS 8 KW w/ pf .8 lag

a) FIND S

b) FIND IMPEDANCE OF THE LOAD

SOLN

$$\textcircled{a} \quad P = |S| \cos \theta \quad \cos \theta = 0.8 \quad \theta = 36.87^\circ$$

$$8 \text{ KW} = |S| (0.8)$$

$$\sin \theta = 0.6$$

$$|S| = 10 \text{ KVA}$$

$$Q = |S| \sin \theta = 10 \text{ KVA} (.6) = 6 \text{ KVAR}$$

$$S = (8 + j6) \text{ KVA}$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$8000 = 240 V I_{rms} (0.8)$$

$$I_{rms} = \frac{8000}{240(0.8)} = 41.67 \text{ Amps}$$

$$|Z| = \left| \frac{V_{rms}}{I_{rms}} \right| = \frac{240}{41.67} = 5.76$$


$$\angle \theta_z = \angle \theta_v - \theta_i = 36.87$$

$$Z = 5.76 \angle 36.87 = \boxed{4.608 + j3.456 \Omega = Z}$$

Ex INDUSTRIAL LOAD USES 88 kW @ $pf = .707$ lag.
FROM 480 Vrms LINE

a) FIND POWER NEEDED FROM Power Co.

b) if $pf = 0.90$

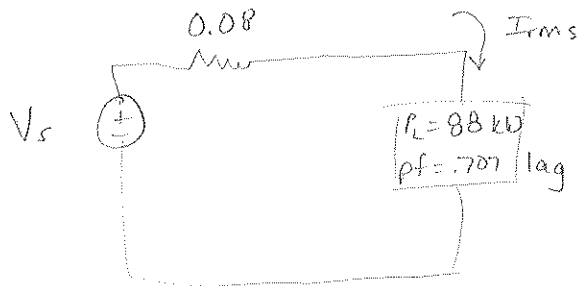

$$P_L = 88 \text{ kW} = I_{rms} V_{rms} (pf)$$

$$88 \text{ kW} = I_{rms} (480) (.707)$$

$$I_{rms} = 259.3 \text{ A}$$


$$P_s = I_{rms}^2 (R) + 88 \text{ kW}$$

$$P_s = 93.38 \text{ kW}$$

b) $pf = 0.90$ $I_{rms} = 203.7 \text{ A}$

$$P_s = 91.32 \text{ kW}$$

Complex Power.

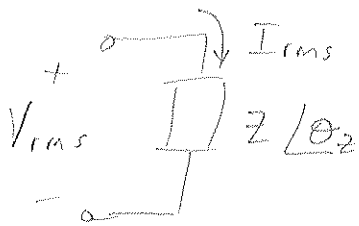

$$S = V_{rms} I_{rms}^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

Real power


reactive
quadrature.

$$S = P + jQ$$

$$P = \text{Re}(S) = V_{rms} I_{rms}$$

FREQUENCY CONTENT OF A SIGNAL

- How fast sample?
- BANDWIDTH

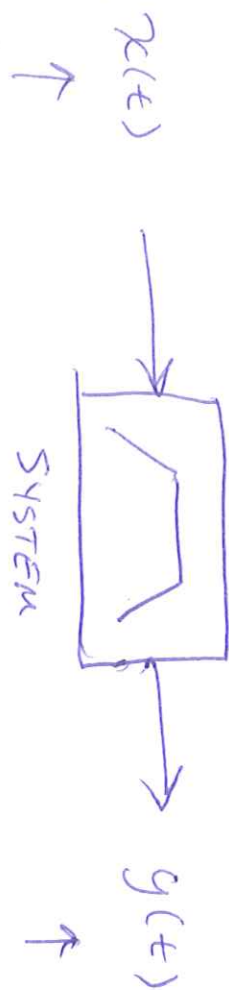

SIGNAL

BANDWIDTH


RANGE OF
FREQUENCIES
voice $\rightarrow 60 \rightarrow 12\text{kHz}$

SYSTEM
FILTER



BANDWIDTH

$f_0 \rightarrow f_{H1}$
 f_{L0}

$BW = f_{H1} - f_{L0}$

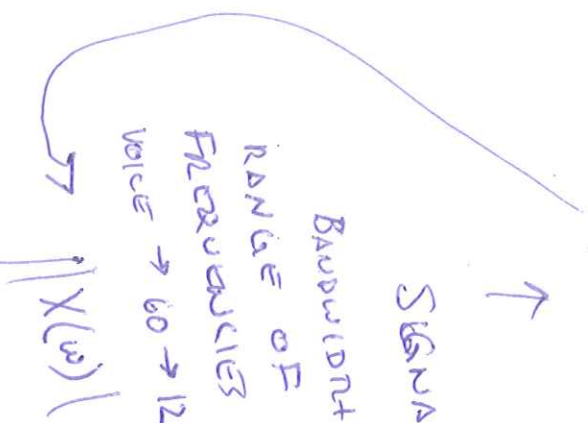

$|X(\omega)|$




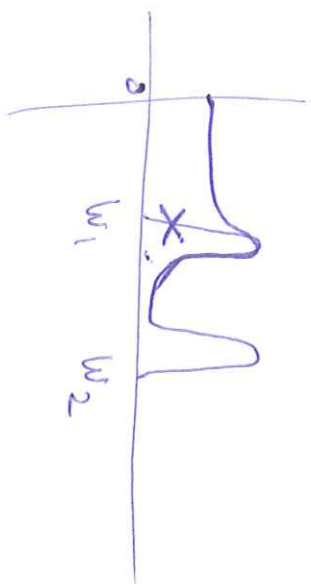
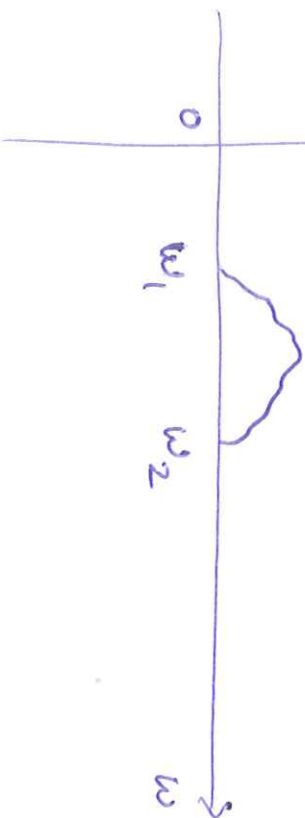


$$Z_L = j\omega L = sL$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{sC}$$



RESONANT CIRCUITS

RC

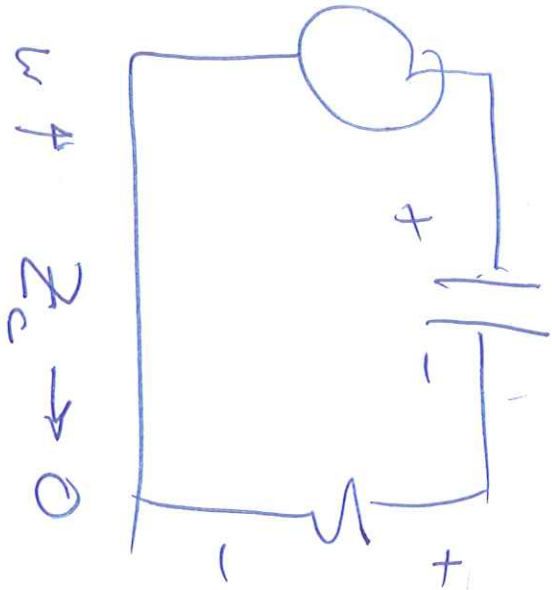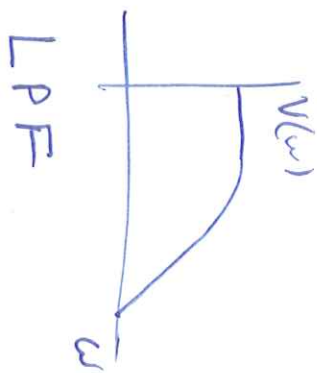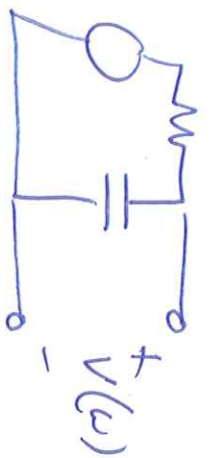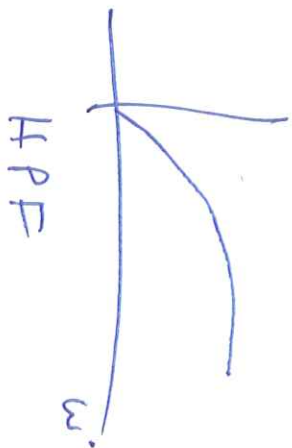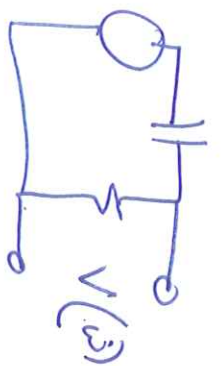


$$\omega \uparrow Z_C \rightarrow 0$$

$$V_R \rightarrow V_S$$

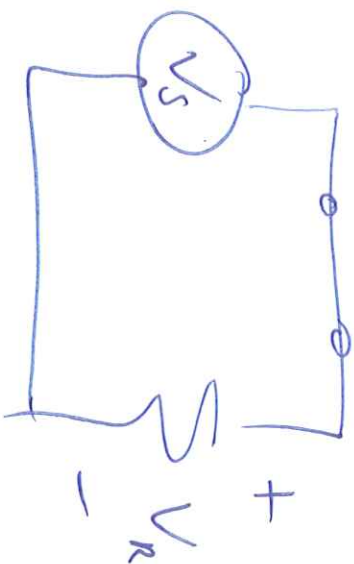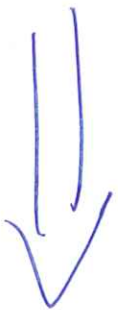



$$\frac{V_{out}}{V_{in}}(\omega) =$$

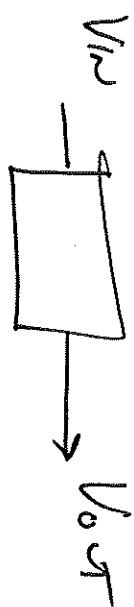

$$V_{out} = V_{in} \left(\frac{Z_c}{Z_c + R} \right) \quad \text{VOLTAGE DIVIDER}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + j\omega RC}$$



$$\omega \rightarrow 0 \quad \frac{V_{out}}{V_{in}} = 1 \quad \angle \frac{V_{out}}{V_{in}} = 0^\circ \quad \angle \frac{V_{out}}{V_{in}} = 0^\circ - 90^\circ = -90^\circ$$

$$\omega \rightarrow \infty \quad \frac{V_{out}}{V_{in}} \rightarrow 0 \quad \angle \frac{V_{out}}{V_{in}} = 180^\circ$$

$$\omega = \frac{1}{RC} \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$


$\omega = \frac{1}{RC} \equiv \text{Breakpoint}$

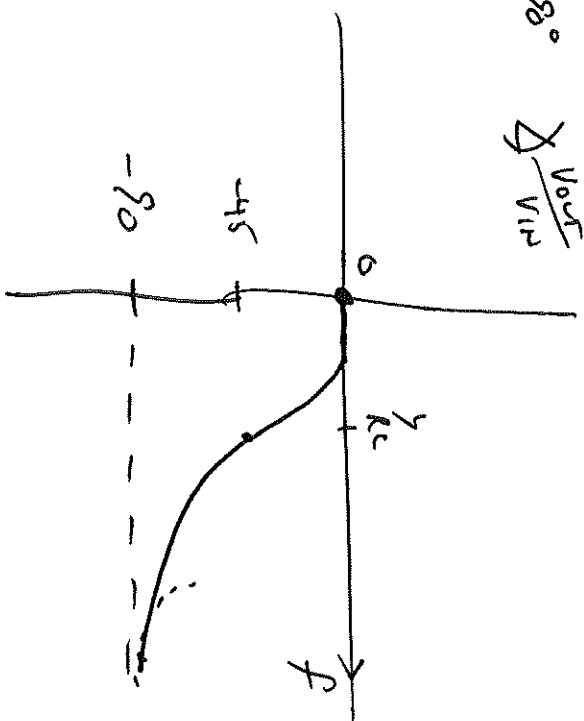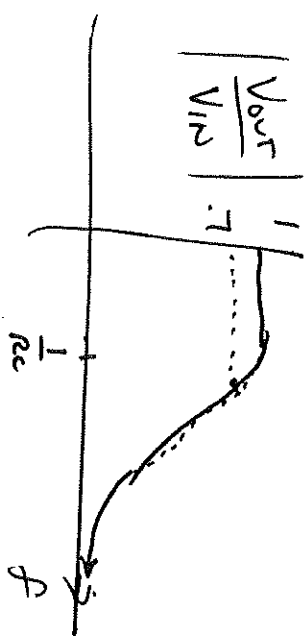
$$\angle \frac{1}{1+j} = \frac{0^\circ}{45^\circ} = 0^\circ - 45^\circ = -45^\circ$$



Low Pass Filter

$\frac{1}{1+j\omega RC}$

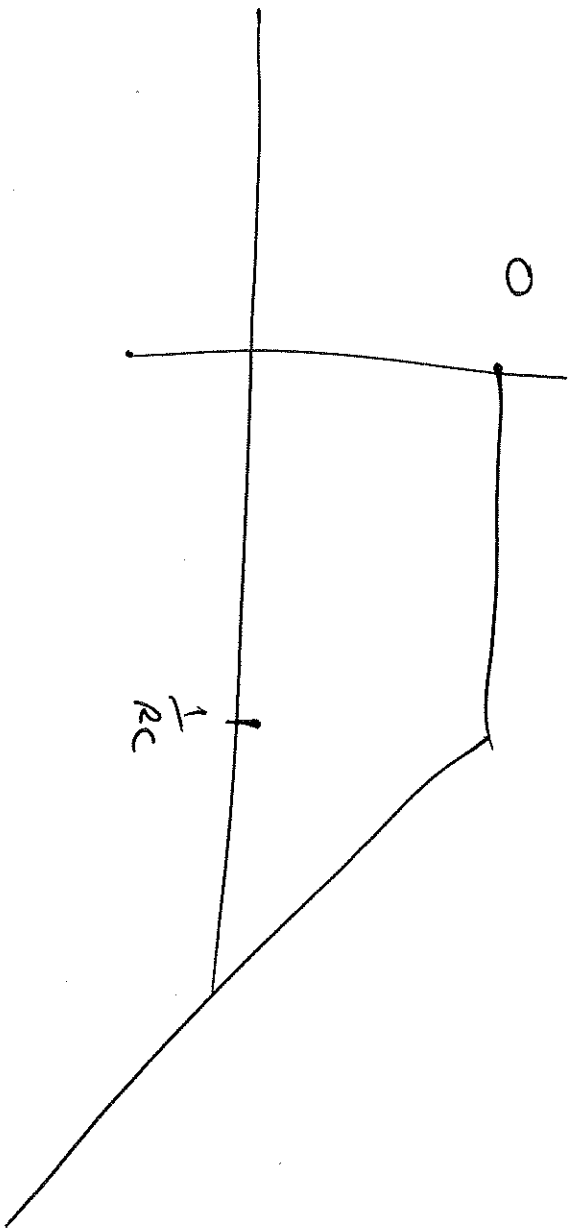

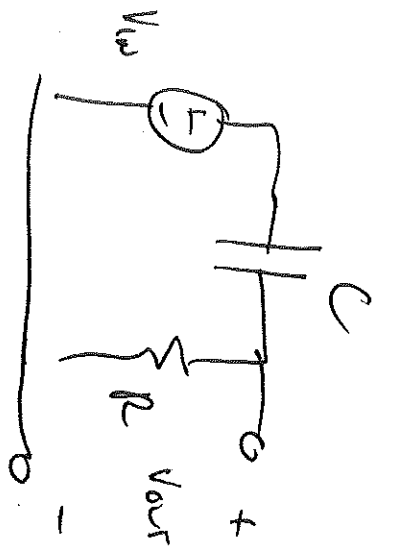



$$\omega \rightarrow 0$$

$$\omega \rightarrow \infty$$

$$\omega \rightarrow \frac{1}{RC}$$

$$V_{out} = V_{in} \frac{R}{R + \frac{1}{j\omega C}}$$
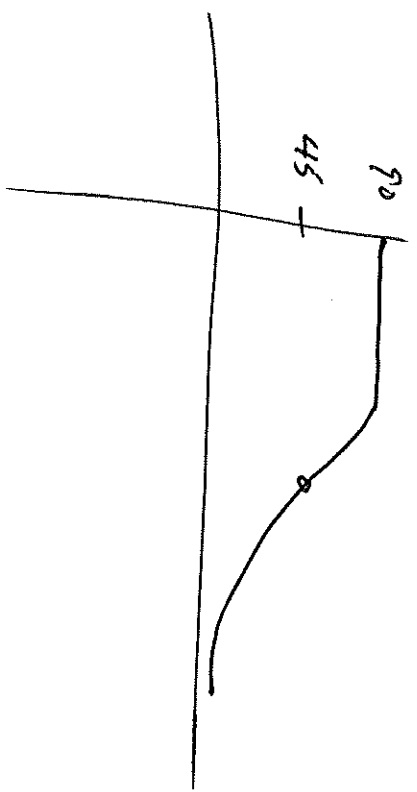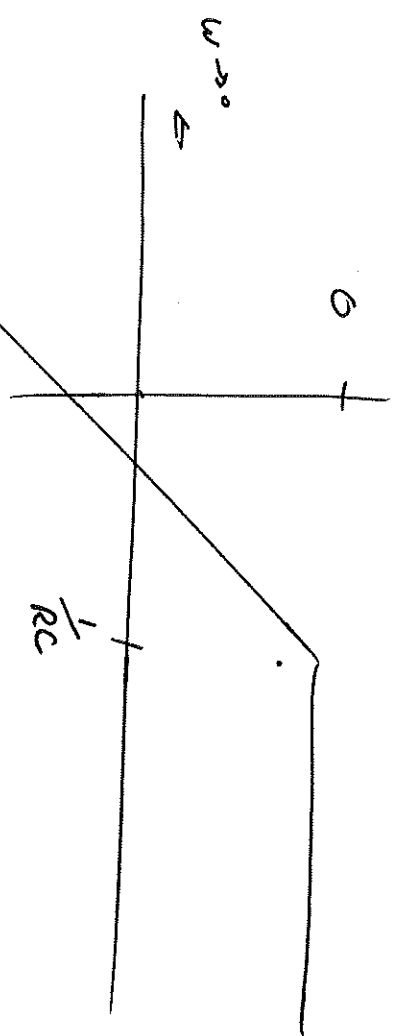
$$\frac{V_{out}}{V_{in}} = \frac{j\omega RC}{j\omega RC + 1}$$



Midterm Thurs July 2

Fri 5 Sat Wed July 1

5-Power 6 7



High Fidelity - clean, quality

attributes of sound

response EAR

transfer functions

Gain vs f
Amplifier

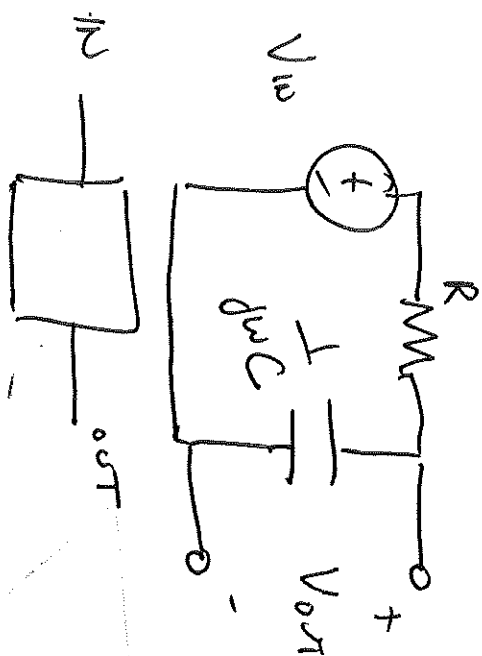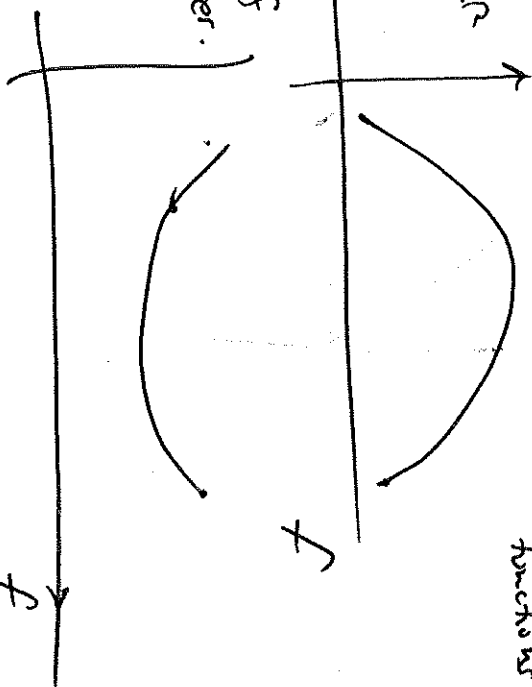



$\frac{V_{out}}{V_{in}} = \text{transfer Fcn}$

$= 1$ unity gain constant



$= 5$

$V_{out} = 5 V_{in}$ AMPLIFIER

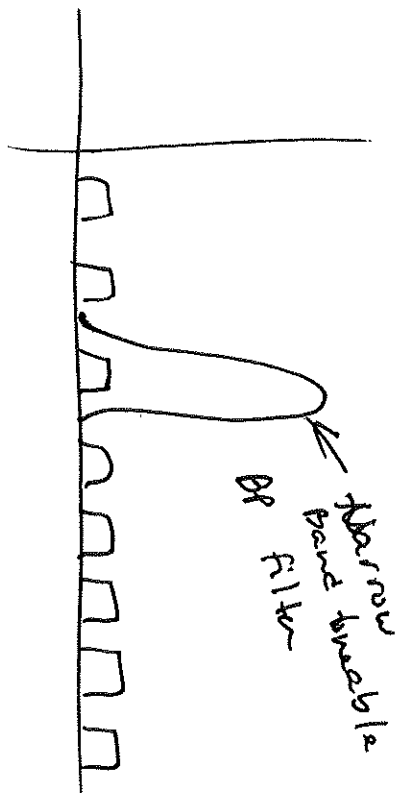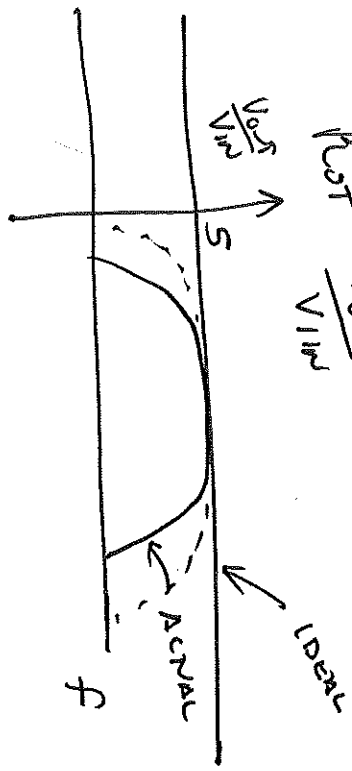$R_{out} \frac{V_{out}}{V_{in}} \text{ vs } f$



SERIES Resonance Ckts

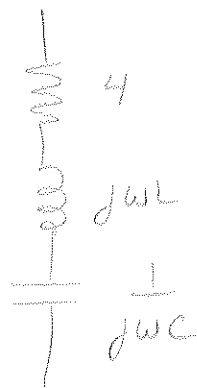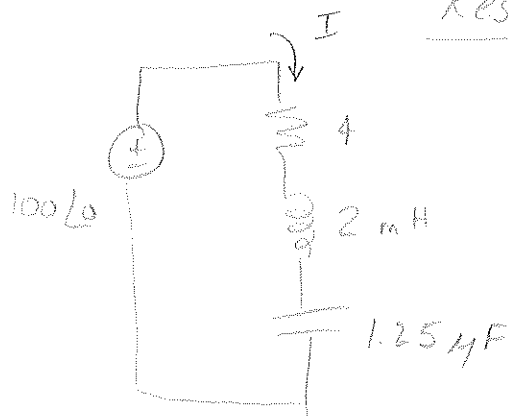

$$Z_T = R + j\omega L - j \frac{1}{\omega C}$$

$$= R + j \left(\omega L - \frac{1}{\omega C} \right)$$

① $\omega L = \frac{1}{\omega C}$

$$\omega_o^2 = \frac{1}{LC}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$


$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow Z_T = R$$

$|Z_T|$ IS MINIMUM

I IS MAXIMUM

$|V_L| = |V_C|$ BUT ARE 180° OUT OF PHASE

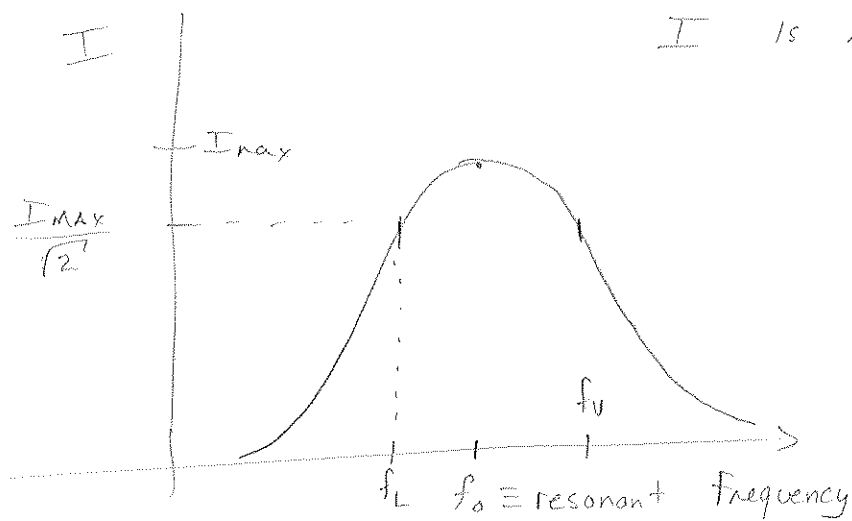


$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o C R}$$

Quality factor

$$BW = \frac{\omega_o}{Q}$$

$$BANDWIDTH = f_U - f_L$$

EX

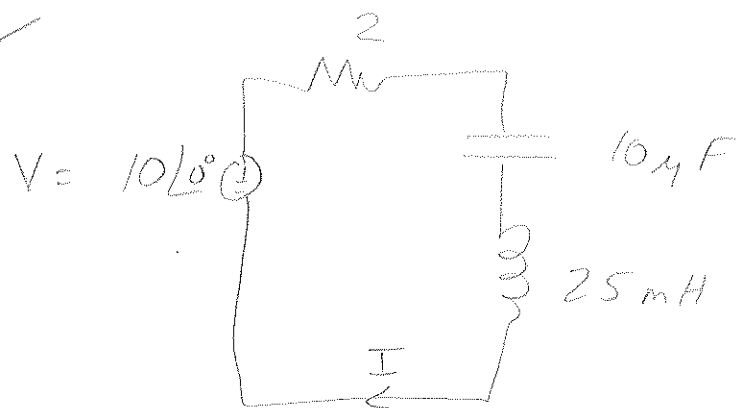

Find ω_0, Q

V_C, V_L
 I
@ ω_0

$$Z_T = R + j\omega L - \frac{1}{j\omega C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2000$$

$$\begin{aligned} \text{@ } \omega_0 \quad I &= \frac{V}{R} \quad \text{B/c } j\omega L - \frac{1}{j\omega C} = 0 \\ &= 5 \angle 0^\circ \end{aligned}$$

$$V_R = I(2) = 10 \angle 0^\circ$$

$$V_L = j\omega L I = 250 \angle 90^\circ$$


$$V_C = \frac{1}{j\omega C} (I) = 250 \angle -90^\circ$$

$$Q = \frac{\omega_0 L}{R} = 25$$

NOTICE: $|V_L| = \omega_0 L |I| = \frac{\omega_0 L}{R} |V_S| = Q |V_S|$

$$|V_C| = \frac{1}{\omega_0 C} |I| = \frac{1}{\omega_0 C R} |V_S| = Q |V_S|$$

Ex

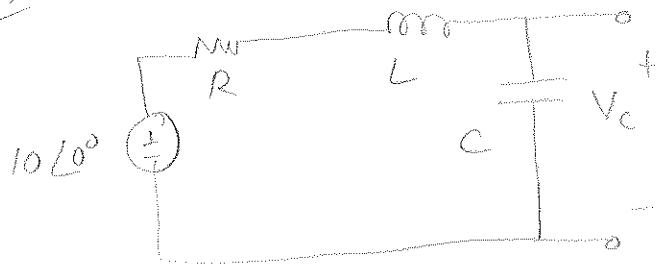

Ckt MUST HAVE:

$$f_0 = 1000 \text{ Hz}$$

$$L = 0.02 \text{ H}$$

$$R = \cancel{0.63} 0.63$$

CHOOSE C FIND V_c @ Resonance.
 Q

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = 1.27 \mu\text{F}$$

$$\omega_0 = 6275 \text{ rad/s}$$

$$Q = \frac{\omega_0 L}{R} = \frac{2\pi(1000)(0.02 \text{ H})}{0.63} = 200$$

At Resonance:

$$j\omega L - \frac{1}{j\omega C} = 0$$

$$Z_T = R$$

$$I = \frac{10\angle 0^\circ}{0.63} = 15.87 \angle 0^\circ$$


$$Z_C = \frac{1}{j\omega C} = \frac{1}{2\pi f C}$$

$$V_c = I Z_C = 6.28 \angle 0^\circ \left(\frac{1}{2\pi(1000)(1.27 \mu\text{F})} \right) \cancel{\angle -90^\circ}$$
$$= 15.87 \angle 0^\circ (125.3 \angle -90^\circ)$$

$$V_c = \frac{V_s}{R} \left(\frac{1}{2\pi f C} \right) = 2000$$

$$\left(\frac{1}{2\pi f C} \right)$$

Parallel Resonance

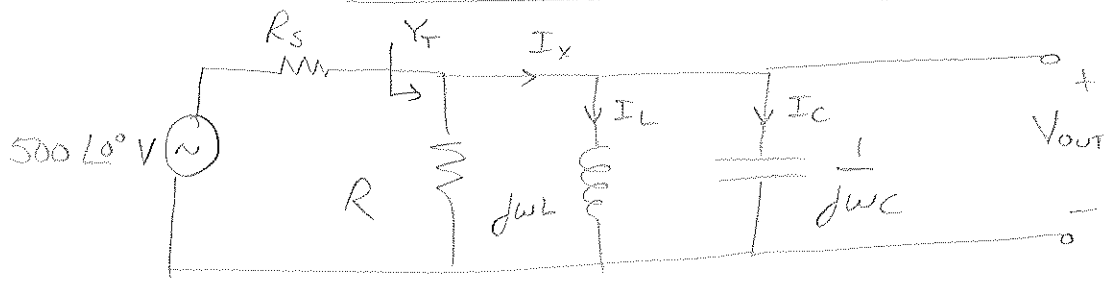

$$Y_T = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$Y_T = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$@ \omega C = \frac{1}{\omega L}$$

$$\omega_o^2 = \frac{1}{LC}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$


$$f_o = \frac{1}{2\pi LC} \Rightarrow Y_T \text{ IS MINIMUM}$$

$$Z_T \text{ IS MAXIMUM}$$

$$V_{out} \text{ IS MAXIMUM}$$

$$|I_L| = |I_C| \text{ BUT ARE } 180^\circ \text{ OUT OF PHASE}$$


$$\therefore I_x = 0$$

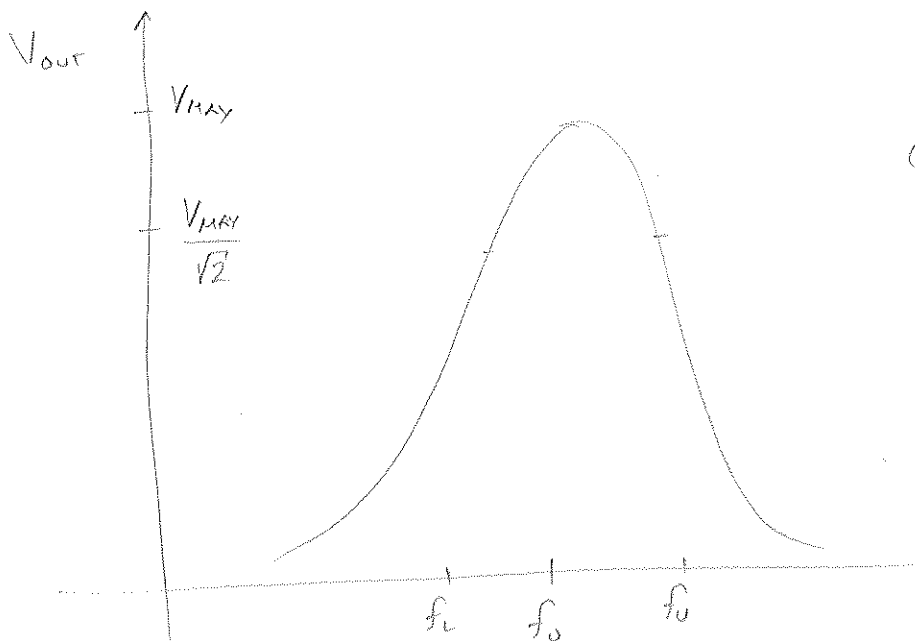

$$Q = \frac{R}{\omega_o L} = \omega_o RC$$

$$BW = \frac{\omega_o}{Q}$$

$$BW = f_U - f_L$$

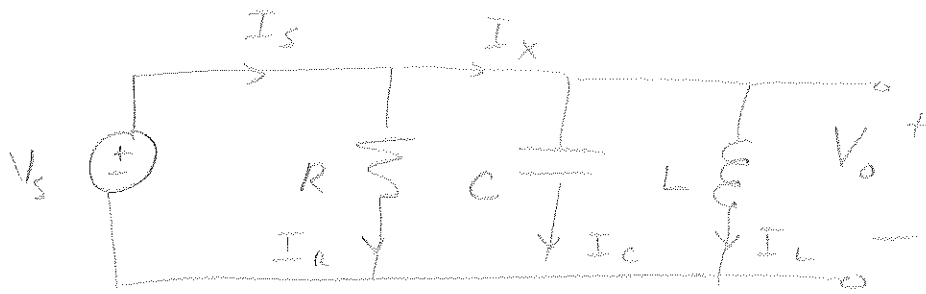

$$V_s = 120 \angle 0^\circ \quad R = 100 \quad C = 600 \mu F \quad L = 120 \text{ mH}$$

FIND ALL I , V_o @ Resonance.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 117.85 \text{ rad/s}$$

$$Y_C = j\omega_0 C = j70.7 \times 10^{-3}$$

$$Y_L = \frac{1}{j\omega_0 L} = -j70.7 \times 10^{-3}$$

$$I_R = \frac{V_s}{R} = \frac{120 \angle 0^\circ}{100} = 1.2 \angle 0^\circ$$

$$I_C = V_s Y_C = 8.49 \angle 90^\circ$$

$$I_L = V_s Y_L = 8.49 \angle -90^\circ$$

$$I_s = I_R + I_C + I_L = 1.2 \angle 0^\circ = I_s$$

$$V_o = V_s \quad (\text{OF COURSE})$$